

Assignment 2

Due date: 8th October 2013

Value: 20%

Marking scheme

The distribution of marks is given in the table below.

The student should provide some explanation of how he/she arrives at an answer. This explanation can be in the form of an equation that the student states or it could be in the form of a brief description of his/her reasoning.

The student will score full marks (as per the table below) if he/she gives the right answer together with a correct explanation (or equation).

For each part, the student can lose up to 35% of the marks if the answer is right, but no explanation is given or the explanation is inadequate.

For each part, the student will be able to score up to 80% of the marks if the answer is wrong but the explanation is correct or partly correct.

Question	(a)	(b)	(c)	(d)	(e)	Total
1	5	5	5	5		20
2	4	4	4	4	4	20
3	4	4	4	4	4	20
4	5	5	5	5		20
5	5	5	5	5		20
6	5	5	5	5		20
7	10	10				20
8	5	5	5	5		20
9	4	4	4	4	4	20
10	4	4	4	4	4	20
Total marks						200

Question 1

This question relates mainly to **Module 7** phase-controlled thyristor converters and the third objective in the course specification.

Use the waveform template given in your introductory book.

Refer to **figure 7.10** of your study book.

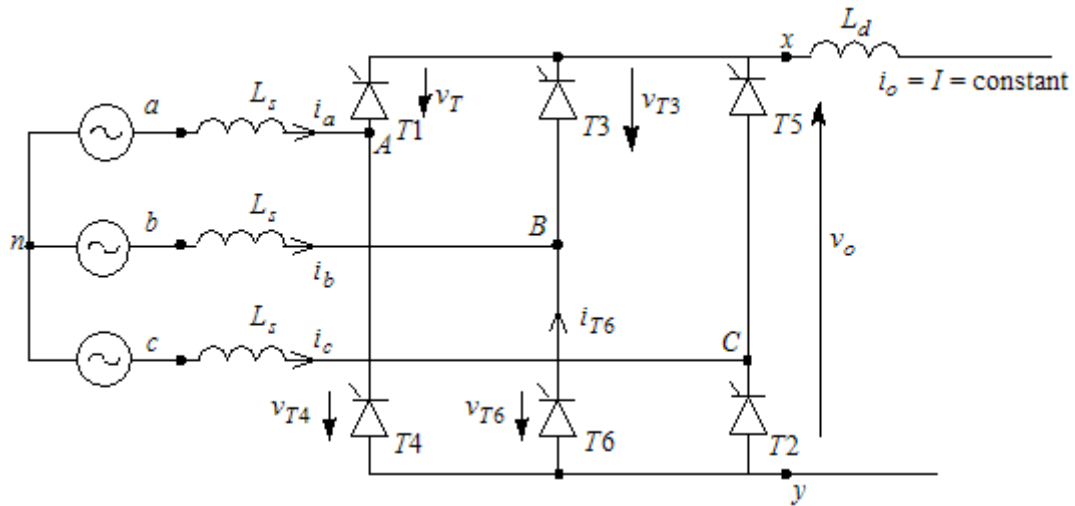


Figure 7.10: Three-phase thyristor converter (L_s – supply inductance)

Assume all components are ideal.

$$v_{an} \text{ (in volts)} = 155.6 \sin \omega t$$

$$\omega = 120 \pi \text{ rad/s}$$

$$I = 20 \text{ A}$$

$$\alpha = \text{delay angle} = 75^\circ$$

For $L_s = 0 \text{ mH}$

- (a) Calculate the mean value of v_o
- (b) Sketch waveform for v_o , v_{T3} and i_{T5}

For $L_s = 0.5\text{mH}$

- (c) Calculate the mean value of v_o
- (d) Sketch waveform for v_o , v_{T3} and i_{T5}

Question 2

This question relates mainly to **Module 7** phase-controlled thyristor converters and the third objective in the course specification.

Refer to **figure 7.24** of your study book.

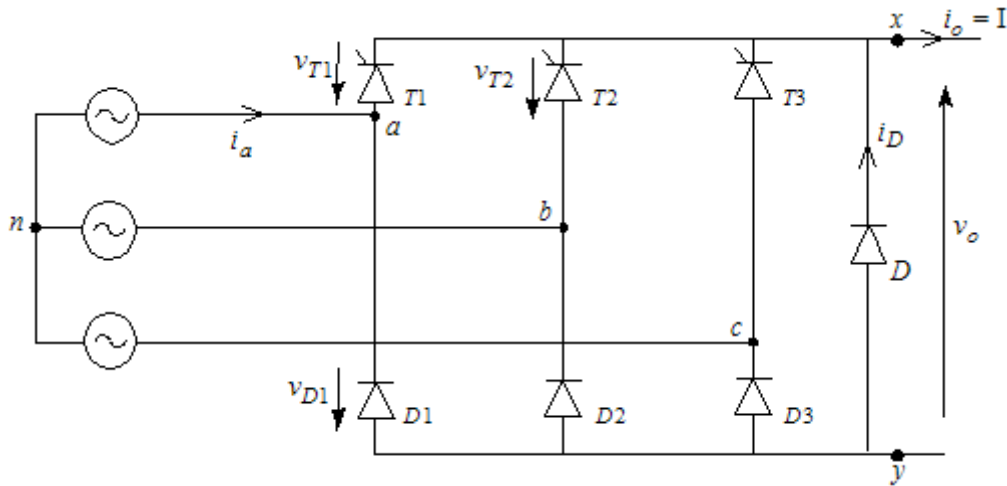


Figure 7.24: Three-phase half controlled rectifier

Assume all components are ideal.

$$v_{an} \text{ (Volts)} = 311 \sin \omega t$$

$$\omega = 100 \pi \text{ rad/s}$$

$$I = 20 \text{ A}$$

$$\alpha = \text{delay angle}$$

For delay angle $\alpha = 30^\circ$ sketch waveforms for:

(a) v_o and v_{T1}

(b) i_a and i_D

For delay angle $\alpha = 105^\circ$ sketch waveforms for:

(c) v_o and v_{T1}

(d) i_b and i_D

(e) Calculate the rms value of i_D for delay angle $\alpha = 105^\circ$.

Question 3

This question relates mainly to **Module 8** switch-mode inverters and the third objective in the course specification.

Refer to the circuit in **figure 8.12** of the study book.

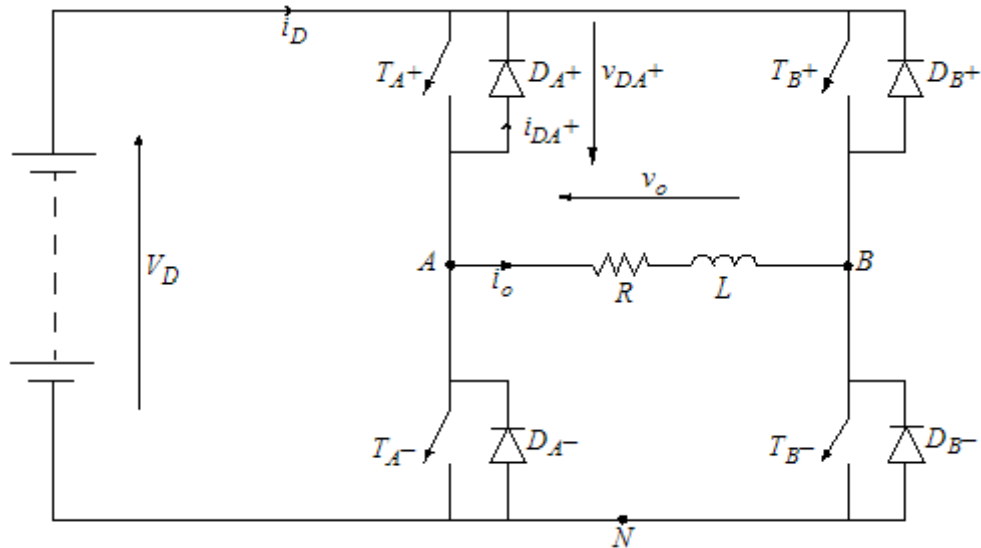


Figure 8.2: Single-phase square wave bridge inverter – R-L load

Assume all components are ideal and v_o is a square wave (unmodified).


$$V_D = 400 \text{ V}; \quad R = 10 \text{ } \Omega; \quad L/R = 25 \text{ ms}; \quad T = 10 \text{ ms}$$

- Calculate \hat{I}_o
- Sketch waveforms for the current through the diode D_{B+}
- Sketch waveforms for the voltage across the diode D_{B+}
- For what fraction of the period does D_{B+} conduct?
- Calculate the rms value of the fundamental component of i_o .

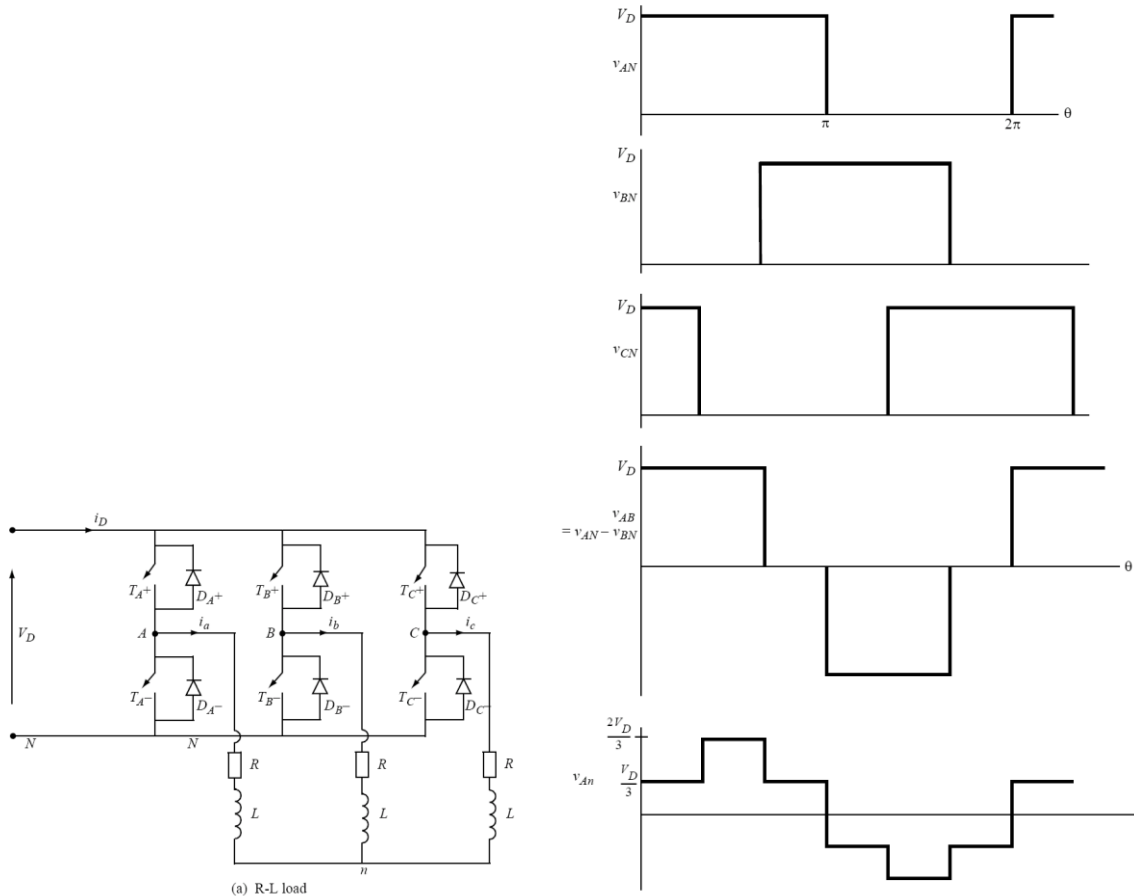Question 4

This question relates mainly to **Module 8** switch-mode inverters and the third objective in the course specification.

Refer to the circuit in **figure 8.12(a)** of the study book. The voltage waveforms in **figure 8.13** are applicable. Circuit operation is at steady state. The mean values of i_a , i_b and i_c are all equal to zero.



$V_D = 220$ V, period = 20 ms

For $R = 0$, $L = 0.1$ H,

- (a) Sketch waveforms for v_{CN} and i_c .
- (b) Calculate the peak value of i_c and the rms value of the fundamental component of i_c

For $R = 20\Omega$, $L = 0$ H,

- (c) Sketch waveforms for v_{CN} and i_c
- (d) Calculate the peak value of i_c and the rms value of the fundamental component of i_c

Question 5

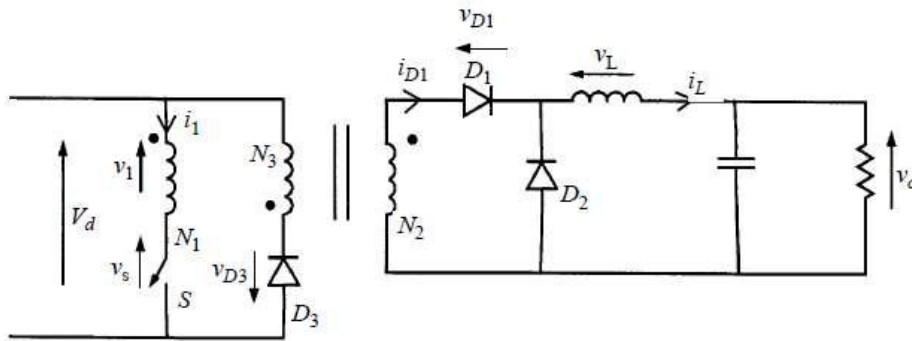


Figure 9.5

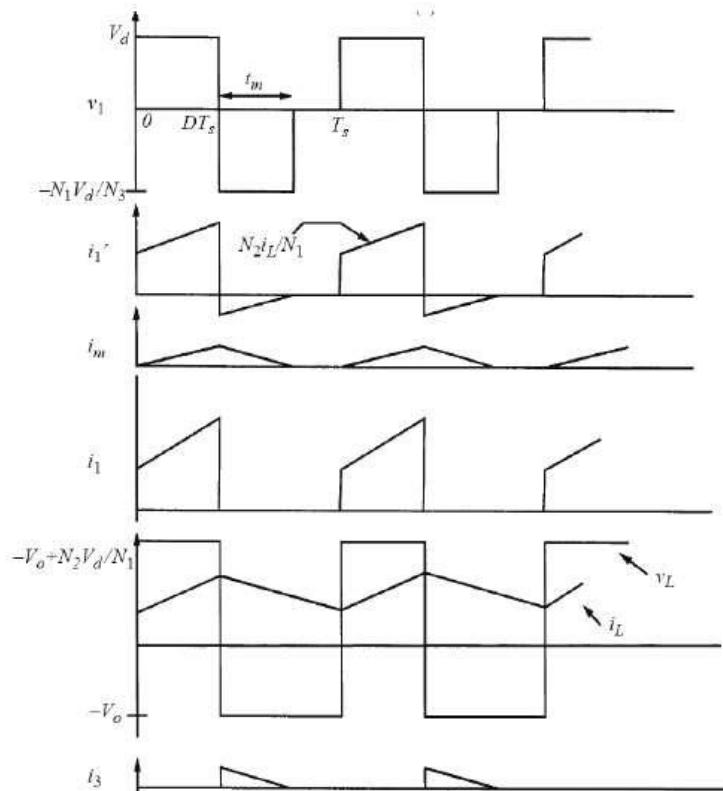


Figure 9.7 (b)

$V_d = 230\text{V}$; $V_o = 80\text{V}$; $1/T_s = 15\text{kHz}$; $N_3 = N_1$; $L = 200\mu\text{H}$; $C = 18\mu\text{F}$.

- Calculate the minimum allowable value of N_2/N_1
- Estimate the peak to peak ripple in v_o . Assume $N_1 = N_2$
- Sketch waveforms for v_{D3}
- Sketch waveforms for i_{D3} .

Question 6

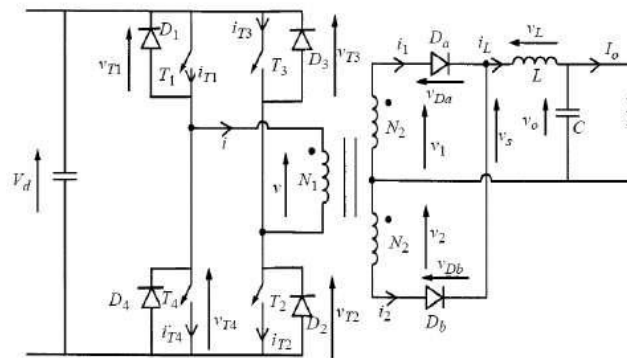


Figure 9.13

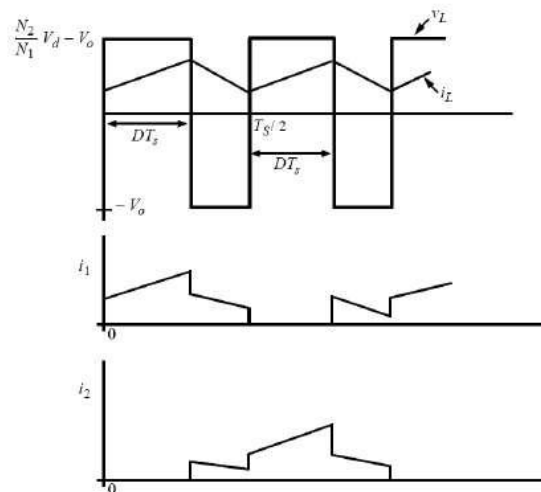


Figure 9.13c

$V_d = 300\text{V}$; $I_o = 5\text{A}$; $V_o = 48\text{V}$; $1/T_s = 20\text{ kHz}$; $N_2/N_1 = 0.25$

- Calculate the value of D .
- Calculate the minimum value of L , if the peak to peak ripple content in i_L is to be maintained below 15% of I_L .
- Sketch waveforms for v_{T2} .
- Sketch waveforms for i_{T2} . Indicate the peak value of i_{T2} .

You may assume equal sharing of voltages by the transistors when all of them are off.

Assume $L = 1.5\text{mH}$.

Question 7

Part (a)

This question relates mainly to **Module 10** drives overview and the fourth objective in the course specification.

A motor is operated at full load and at rated speed for **6 minutes** and then it is operated at no-load for **12 minutes**.

This operating cycle is continuously repeated resulting in motor insulation temperature changing periodically.

As a first approximation the thermal behaviour of the insulation can be modelled as that of a first order system with a thermal time constant τ of **30 minutes** and a thermal resistance of **0.2° C/W**.

Motor power losses at full load = 550 W

Motor power losses at no-load = 220 W

Insulation temperature rise above ambient while the motor is loaded is given by:

$$T = T_1 T_2 e^{-t/\tau}$$

where $t = 0$ at the instant load is applied to the motor.

T_1 is the insulation temperature rise above ambient that would be reached if the motor was to be left fully loaded for a very long time (i.e. t approaches infinity).

Insulation temperature rise above ambient while the motor is running idle is given by:

$$T = T_3 T_4 e^{-t/\tau}$$

where $t = 0$ at the instant load is removed from the motor.

T_3 is the insulation temperature rise above ambient that would be reached if the motor was to be left energised but unloaded for a very long time (i.e. approaches infinity).

Calculate the values of T_1 , T_2 , T_3 , T_4 . Deduce the peak value of the insulation temperature. Sketch motor insulation temperature rise against time.

Part (b)

This question relates mainly to **Module 10** drives overview and the fourth objective in the course specification.

One cycle of the motion profile of a purely inertial load is described below:

Time	Description of motion
0 – 5 s	constant acceleration from 0 rad/s to 300 rad/s
5 s – 10 s	constant speed at 300 rad/s
10 s – 15 s	constant deceleration from 300 rad/s to 150 rad/s
15 s – 25 s	constant deceleration from 150 rad/s to 0 rad/s
25 s – 30 s	stationary

Combined moment of inertia = 12 kgm².

Neglecting all losses; The load is directly coupled to the motor.

- (a) Calculate the peak torque required from the motor.
- (b) Calculate the rms value of the motor torque.

Question 8

This question relates mainly to **Module 11**. DC adjustable speed drives and the fifth objective in the course specification.

Refer to the circuit in **figure 11.6** of the study book.

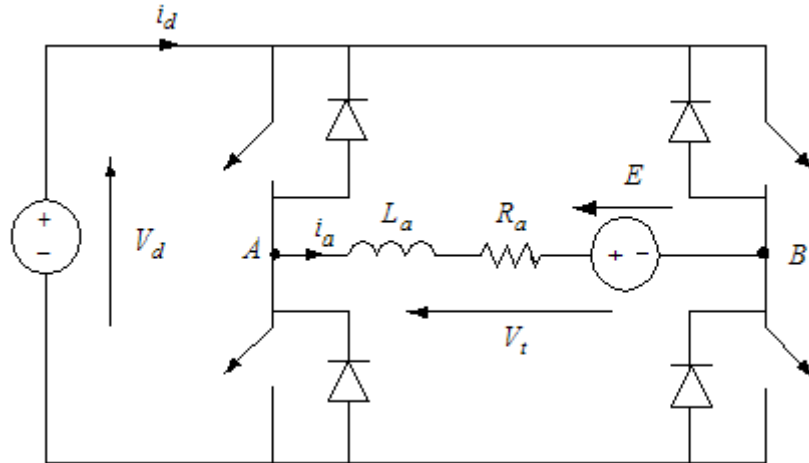


Figure 11.6: Four quadrant DC drive (ϕ_f constant)

Assume all components in the converter are ideal.

$$V_d = 200 \text{ V}; \quad K_E = 0.6 \text{ V/(rad/s)}; \quad L_a = 15 \text{ mH}; \quad R_a = 0.5 \Omega$$

The unipolar control method is used to operate the bridge. Transistor switching frequency is 1.5 kHz.

If speed is 1500 r/min and I_a is 0A draw waveforms for:

(a) v_t and

(b) i_a .

If speed is 1500 r/min, but in reverse direction compared to the above, and I_a is **20 A**.

The motor is in regenerative braking mode, draw waveforms for:

(c) v_t and

(d) i_a . Indicate maximum and minimum values of i_a .

Question 9

This question relates mainly to **Module 11**. DC adjustable speed drives and the fifth objective in the course specification.

Consider the circuit in **figure 11.14(a)** of the study book.

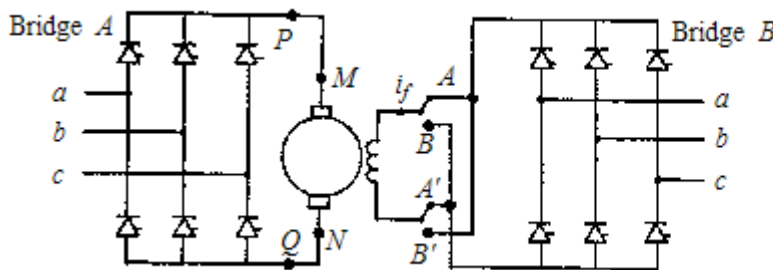


Figure 11.14(a)

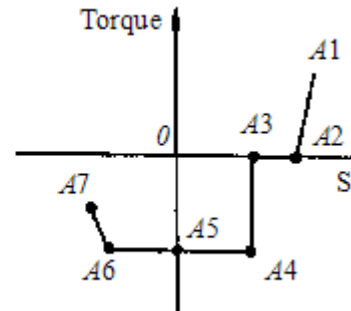


Figure 11.14(b)

The line to line voltage of the three phase AC supply is **415 V**. While motoring at **point A1, figure 11.14(b)**, the load torque, including friction torque is equal to **50 Nm** and the speed is equal to **1000 r/min**. Current limit, positive or negative, is set at **50 A**. Values for some of the motor parameters are given below:

$$K_E = 1.2 \text{ V}/(\text{rad/s}); \quad K_T = 1.8 \text{ Nm/A}; \quad R_a = 0.75 \Omega$$

The values of K_E and K_T correspond to rated field current.

While motoring at **point A7, figure 11.14(b)**, the load torque is **20 Nm** and the speed is **1250 r/min**. Compared to operation at **point A1**, field current has reversed, but its magnitude is unchanged. The magnitude of the field current is equal to its rated value at all times, except during reversal between **point A2** and **point A3** in **figure 11.14(b)**.

Neglect the effect of supply inductance. Assume that there is no speed drop or rise from points **A1** to **A2**, **A3** to **A4** and **A6** to **A7**. There is a ten per cent speed drop from **A2** to **A3**.

Determine the delay angles of **bridge A** during operation at points:

- (a) A1
- (b) A4
- (c) A5
- (d) A6 and
- (e) A7.

Question 10

This question relates mainly to the sixth objective in the course specification.

A 22kW, 440V, 50Hz, 4-pole cage induction motor is part of an adjustable speed drive system. At the base voltage and frequency, the full-load slip is 0.05. It can be assumed that the torque-speed characteristic of the motor is linear in the slip frequency range from –5 Hz to 5 Hz.

Combined moment of inertia of motor and load = 12kgm².

Load torque in Nm = 5 ω where ω is in rad/s.

The steady state operating speed ranges from 900r/min to 1400r/min.

Acceleration is required to be constant at 30rad/s² and deceleration is required to be constant at 60 rad/s².

The drive consists of a voltage source inverter with a three-phase diode rectifier at the front end. The supply voltage may be assumed to be 440V.

Estimate:

- (a) steady state-slip when speed is 1400r/min.
- (b) steady state slip when speed is 900r/min.
- (c) required electromagnetic torque during acceleration and during deceleration.
- (d) maximum DC input current to the inverter during acceleration (assume efficiency of motor-inverter combination is 91%).
- (e) acceleration time from zero speed to 1400r/min.