

a) Convert 0010001010000110 (BCD) into its binary equivalent and then divide it by 100102. Express your result in octal equivalent.

b) Design a half adder circuit using only NAND gates.