

When you have completed your exam and reviewed your answers, click **Submit Exam**. Answers will not be recorded until you hit **Submit Exam**. If you need to exit before completing the exam, click **Cancel Exam**.

**Questions 1 to 25:** Select the best answer to each question. Note that a question and its answers may be split across a page break, so be sure that you have seen the *entire* question and *all* the answers before choosing an answer.

**1.** An inductor rated at 10 mH and a 100  $\Omega$  resistor are in an AC circuit that has a frequency of 100 Hz. What is the inductive reactance at this frequency?

- A. 12.56  $\Omega$
- B. 6.28  $\Omega$
- C. 31.40  $\Omega$
- D. 62.8  $\Omega$

**2.** What is the inductive reactance of a 0.5 H inductor connected with a 1000  $\Omega$  resistor in an AC circuit supplied with 48 VAC at 100 Hz?

- A. 500  $\Omega$
- B. 0.31  $\Omega$
- C. 150.72  $\Omega$
- D. 314  $\Omega$

**3.** A series circuit contains a 30 mH inductor and a 200  $\Omega$  resistor. What is the total circuit current (rounded) if the applied voltage is 60 V and the frequency is 1000 Hz?


- A. 0.84 A
- B. 1.24 A
- C. 0.44 A
- D. 0.22 A

**4.** What is the time constant of a 5 mH inductor in series with 2000  $\Omega$  resistor?

- A. 2.5  $\mu$ s
- B. 10 ms
- C. 5 ms
- D. 10  $\mu$ s

**5.** If an 80 mH inductor is in series with a 220  $\Omega$  resistor in a circuit with a source frequency of 1000 Hz, what will be the phase angle (rounded) of the current with respect to the voltage?

- A. 70°
- B. 50°
- C. 48°
- D. 66°

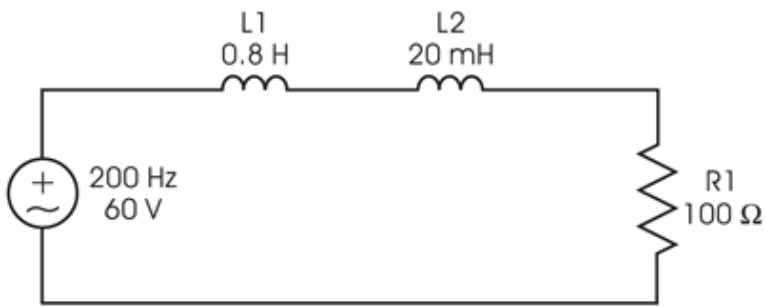


6. What is the inductive reactance of the circuit's two coils as shown in the figure?

- A. 308.98  $\Omega$
- B. 2574.80  $\Omega$
- C. 1029.92  $\Omega$
- D. 20.10  $\Omega$


7. A circuit contains a 20  $\mu\text{H}$  and a 60  $\mu\text{H}$  inductor connected in parallel. These two inductors are in series with a 1000  $\Omega$  resistor. The circuit has a source voltage of 30 VAC at 10,000 Hz. What is the total inductive reactance of this circuit?

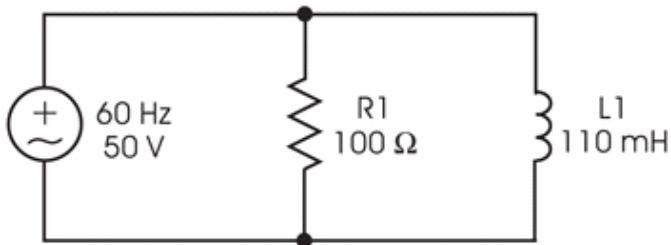- A. 2.43  $\Omega$
- B. 0.942  $\Omega$
- C. 63.6  $\Omega$
- D. 94.2  $\Omega$



8. What is the current through the inductor shown in the figure?

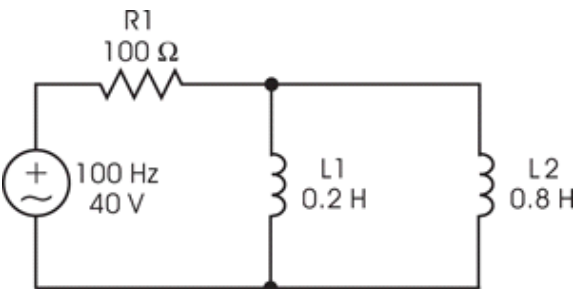- A. 1.45 A
- B. 450.50 A
- C. 0.450 A
- D. 1.21 A




9. What is the impedance of the circuit shown in the figure?

- A. 285.15  $\Omega$
- B. 60.23  $\Omega$

C. 141.76  $\Omega$

D. 70.88  $\Omega$

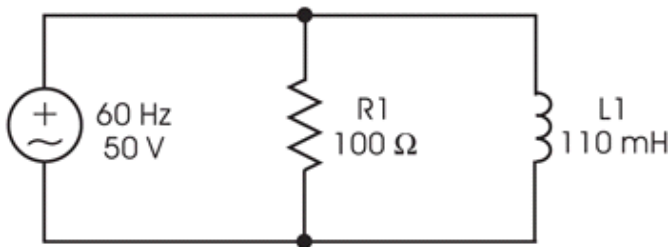

10. What is the total current ( $I_T$ ) of the circuit shown in the figure?

A. 1.71 A

B. 1.50 A

C. 1.31 A

D. 0.88 A

11. A 6 mH, a 2 mH, and a 10 mH inductor are placed in series with a 1000  $\Omega$  resistor in a circuit. The circuit has a source voltage of 60 VAC at 1000 Hz. What is the total inductive reactance of this circuit?

A. 93.80  $\Omega$

B. 86.42  $\Omega$

C. 121.64  $\Omega$

D. 113.04  $\Omega$


12. A 10 mH inductor and a 100  $\Omega$  resistor are connected in parallel. The circuit is supplied with 24 VAC at 2000 Hz. What is the inductive reactance of the inductor?

A. 442.6  $\Omega$

B. 386.2  $\Omega$

C. 125.6  $\Omega$

D. 226.4  $\Omega$

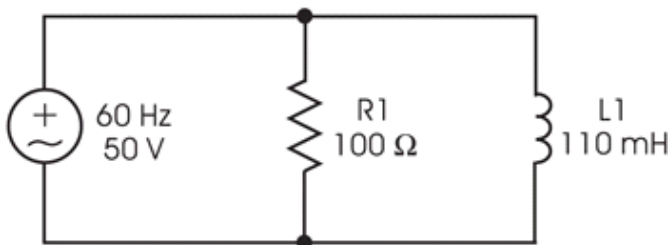

13. What is the inductive reactance of the circuit shown in the figure?

A. 6.91  $\Omega$

B. 41.45  $\Omega$


C. 34.54  $\Omega$

D. 41,448  $\Omega$

14. A circuit contains a 60 mH and a 40 mH inductor connected in parallel. The circuit has a source voltage of 100 VAC and a frequency of 1000 Hz. What is the total inductive reactance (rounded) of the circuit?


A. 173  $\Omega$

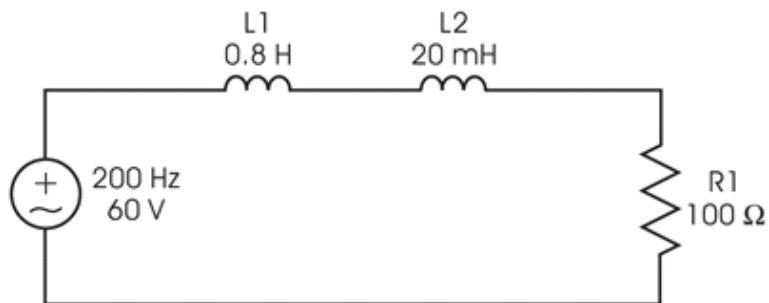- B.  $151 \Omega$
- C.  $194 \Omega$
- D.  $212 \Omega$



15. What is the total circuit current of the circuit shown in the figure?

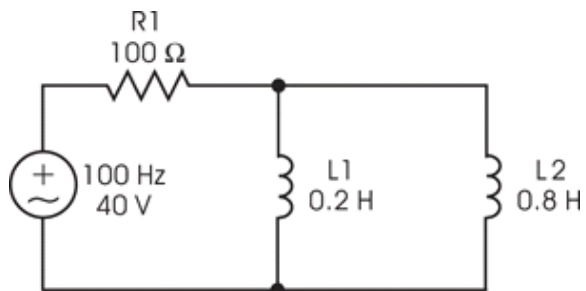- A. 0.19 A
- B. 0.18 A
- C. 0.06 A
- D. 0.04 A



16. What is the approximate lagging phase angle for the current in the circuit shown in the figure?


- A.  $75^\circ$
- B.  $45^\circ$
- C.  $30^\circ$
- D.  $85^\circ$

17. A 10 mH inductor and a  $100 \Omega$  resistor are connected in parallel. The circuit is supplied with 24 VAC at 2000 Hz. What is the phase angle (rounded) of this circuit?

- A.  $49.2^\circ$
- B.  $38.4^\circ$
- C.  $24.6^\circ$
- D.  $28.2^\circ$


18. Which of the following denotes impedance?

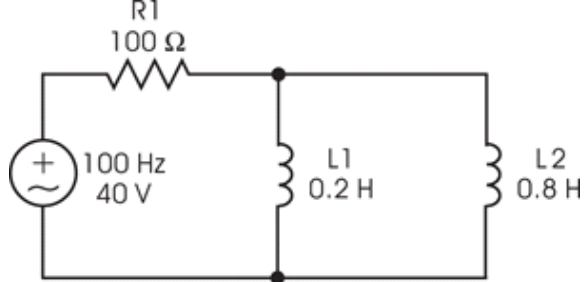- A.  $R$
- B.  $X_L$
- C.  $Z$
- D.  $H$



19. What is the total inductance of the circuit shown in the figure?

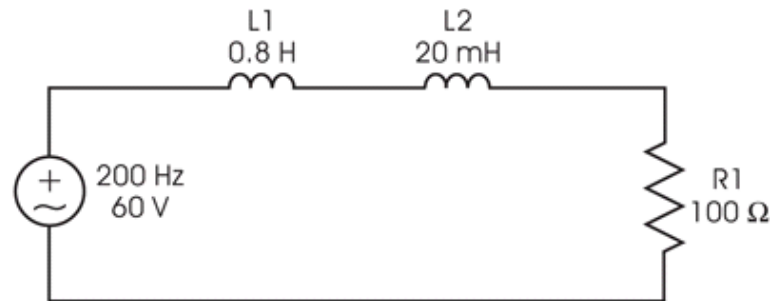- A. 1.0 H
- B. 0.48 H
- C. 0.63 H
- D. 0.16 H



20. What is the total inductance of the circuit shown in the figure?

- A. 0.82 H
- B. 20.80 H
- C. 2.05 H
- D. 51.25 H

21. If you doubled the voltage frequency in an RL series AC circuit, the inductive resistance would

- A. increase by only one quarter.
- B. also double.
- C. remain constant.
- D. decrease by only one half.

22. A 10 mH inductor and a 100 Ω resistor are connected in parallel. The circuit is supplied with 24 VAC at 2000 Hz. What is the impedance (rounded) of the circuit?

- A. 57.38 Ω
- B. 78.23 Ω
- C. 108.71 Ω
- D. 98.16 Ω


23. A circuit has an inductor with an inductive reactance of 230 Ω. This inductor is in series with a 500 Ω resistor. If the source voltage is 24 V, what is the total circuit current (rounded)?

- A. 0.44 A
- B. 0.04 A
- C. 0.18 A

D. 0.22 A

24. Which of the following denotes inductive reactance?

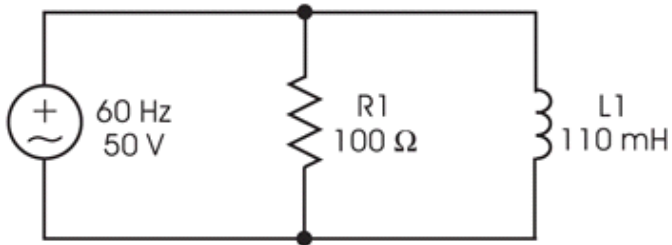- A.  $R$
- B.  $X_L$
- C.  $H$
- D.  $Z$



25. What is the current through the resistor in the circuit shown in the figure?

- A. 5 A
- B. 0.50 A
- C. 0.60 A
- D. 2 A

---

End of exam