

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

NAME: _____ Due: 03/06/2017


**Show your work. Answers without supporting work will not earn full credit.
Ignore all flip-flop sets and resets.**

1. Draw a five D flip-flop Johnson counter. Do not include forbidden state detection. Assuming the flip-flops are initially all ones, show the successive states through the return to all ones.

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

 2. Given the following circuit, generate its state chart and draw its state diagram.




X	Y	A	X ⁺	Y ⁺	Z	D _X	D _Y
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7


PROBLEM #2, Continued:

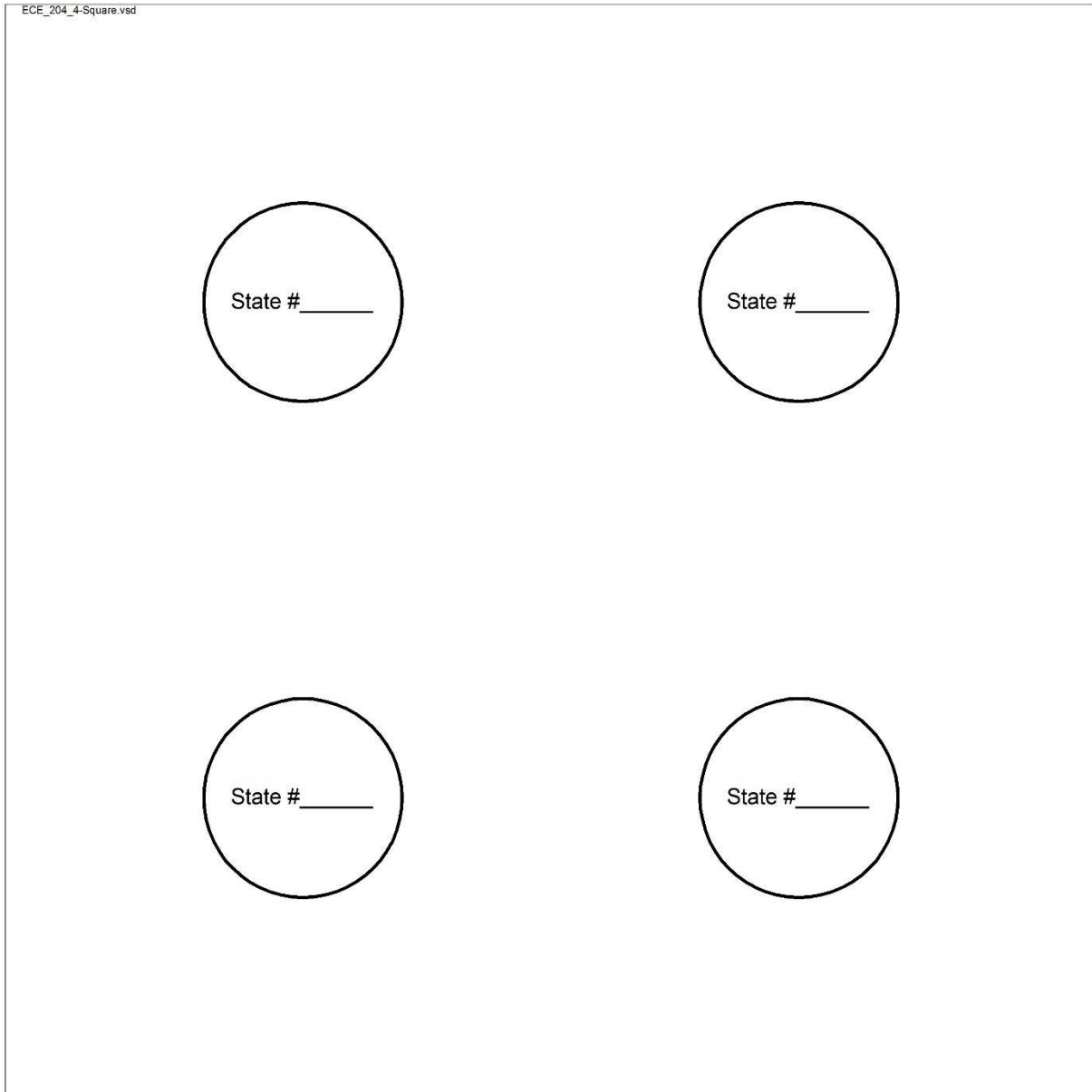

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

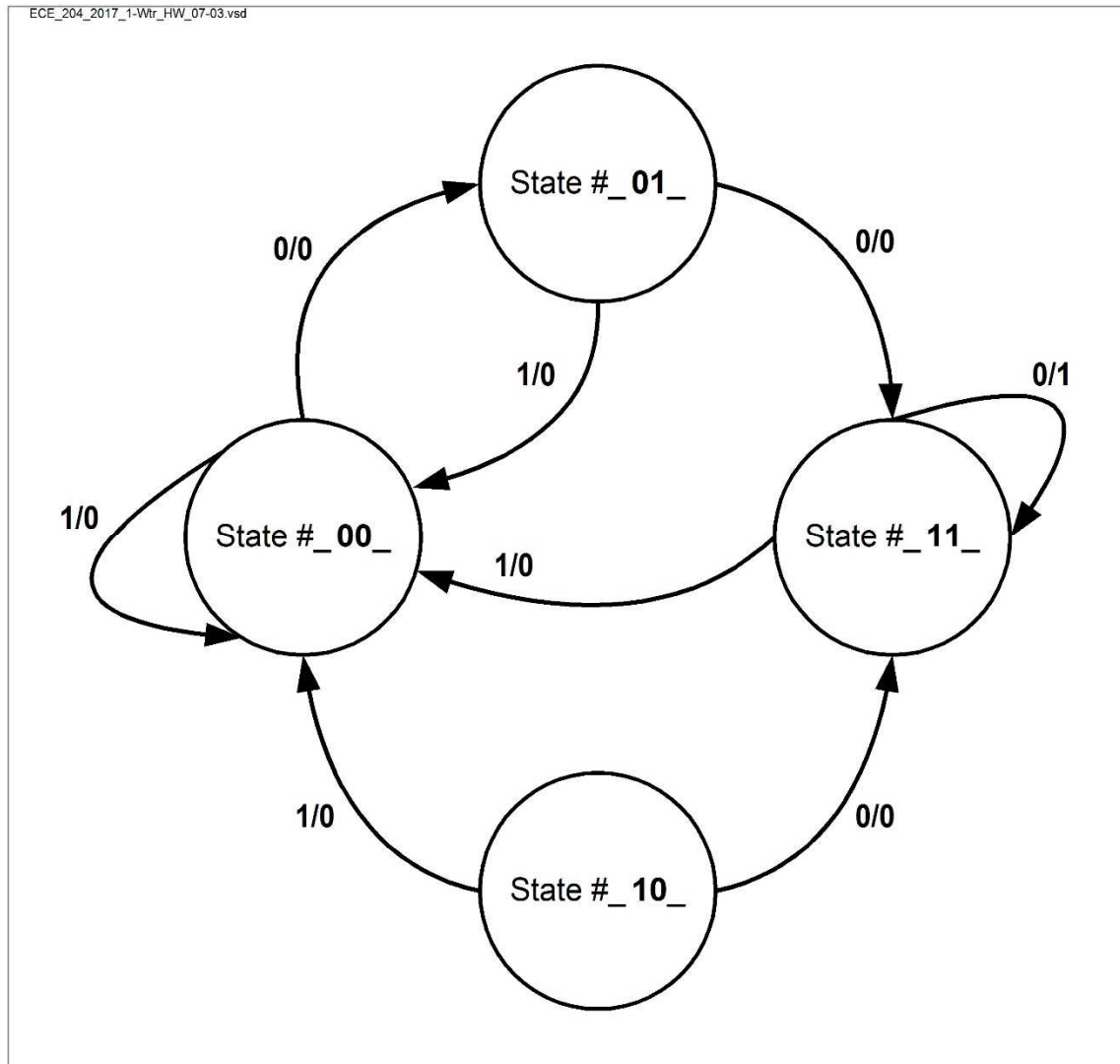3. Given the following state diagram, generate the corresponding state chart including the D inputs. Also give the minimized equations for the D inputs and for the output, **B**. Let the state bits be labeled **X** and **Y**, the input **A** and the output **B**.



ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

PROBLEM #3, Continued:

X	Y	A	X ⁺	Y ⁺	B	D _X	D _Y
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

X/YA	00	01	11	10
0				
1				

X/YA	00	01	11	10
0				
1				

X/YA	00	01	11	10
0				
1				

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

4. Complete the following partial state chart by showing the necessary J and K inputs for the flip flops. Give the minimized equations for the J and K inputs and for the output, and draw the state diagram. The state bits are A and B , the input is C and the output is Z .

A	B	C	A ⁺	B ⁺	Z	J _A	K _A	J _B	K _B
0	0	0	0	1	0				
0	0	1	1	0	1				
0	1	0	0	0	0				
0	1	1	1	1	1				
1	0	0	0	0	0				
1	0	1	1	1	1				
1	1	0	1	0	0				
1	1	1	0	1	1				

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

PROBLEM #4, Continued:

A/BC	00	01	11	10
0				
1				

A/BC	00	01	11	10
0				
1				


A/BC	00	01	11	10
0				
1				

A/BC	00	01	11	10
0				
1				

A/BC	00	01	11	10
0				
1				

ECE 204 Introduction to Digital Logic Bill Nelson
Homework #7


PROBLEM #4, Continued:

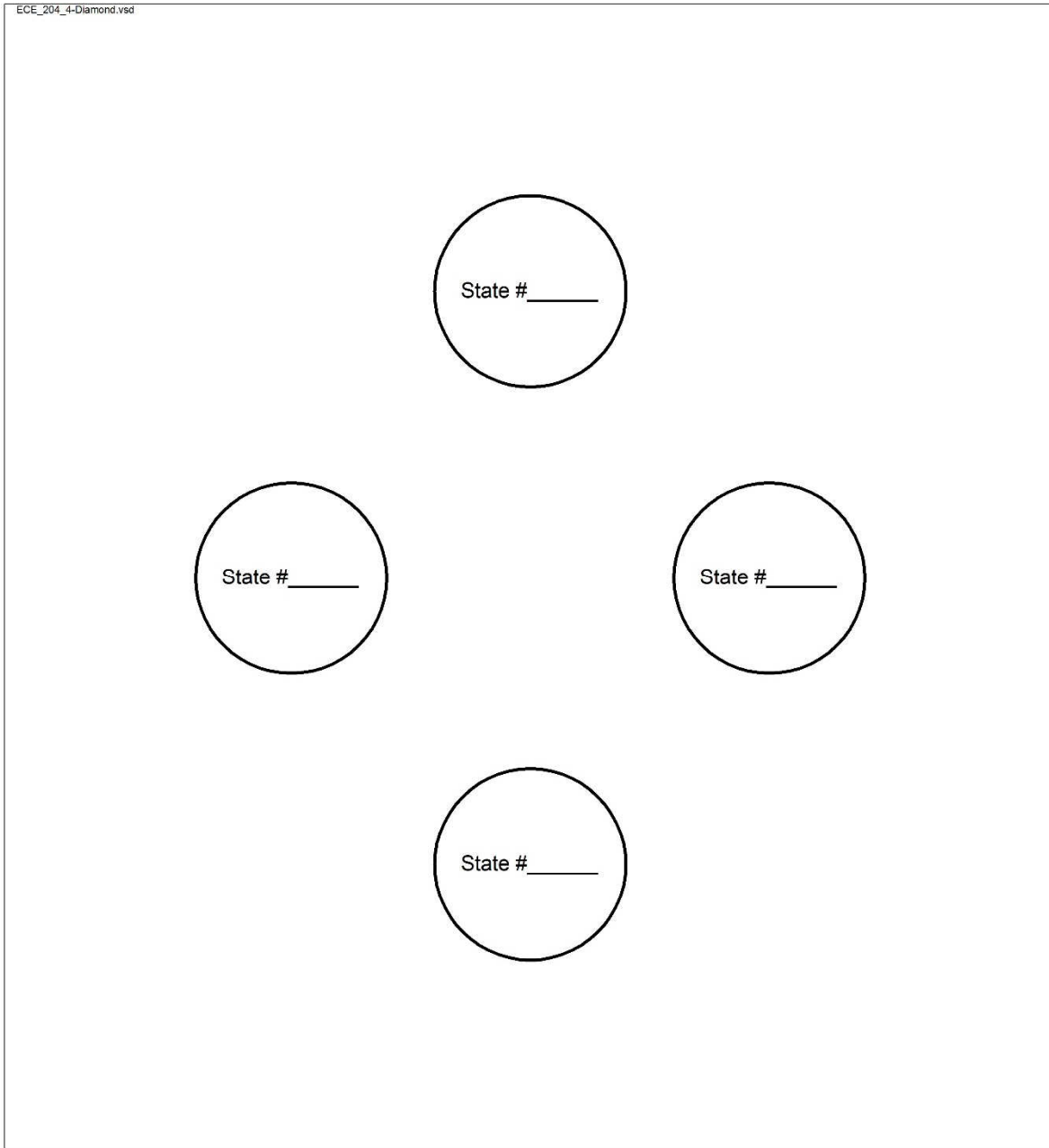

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

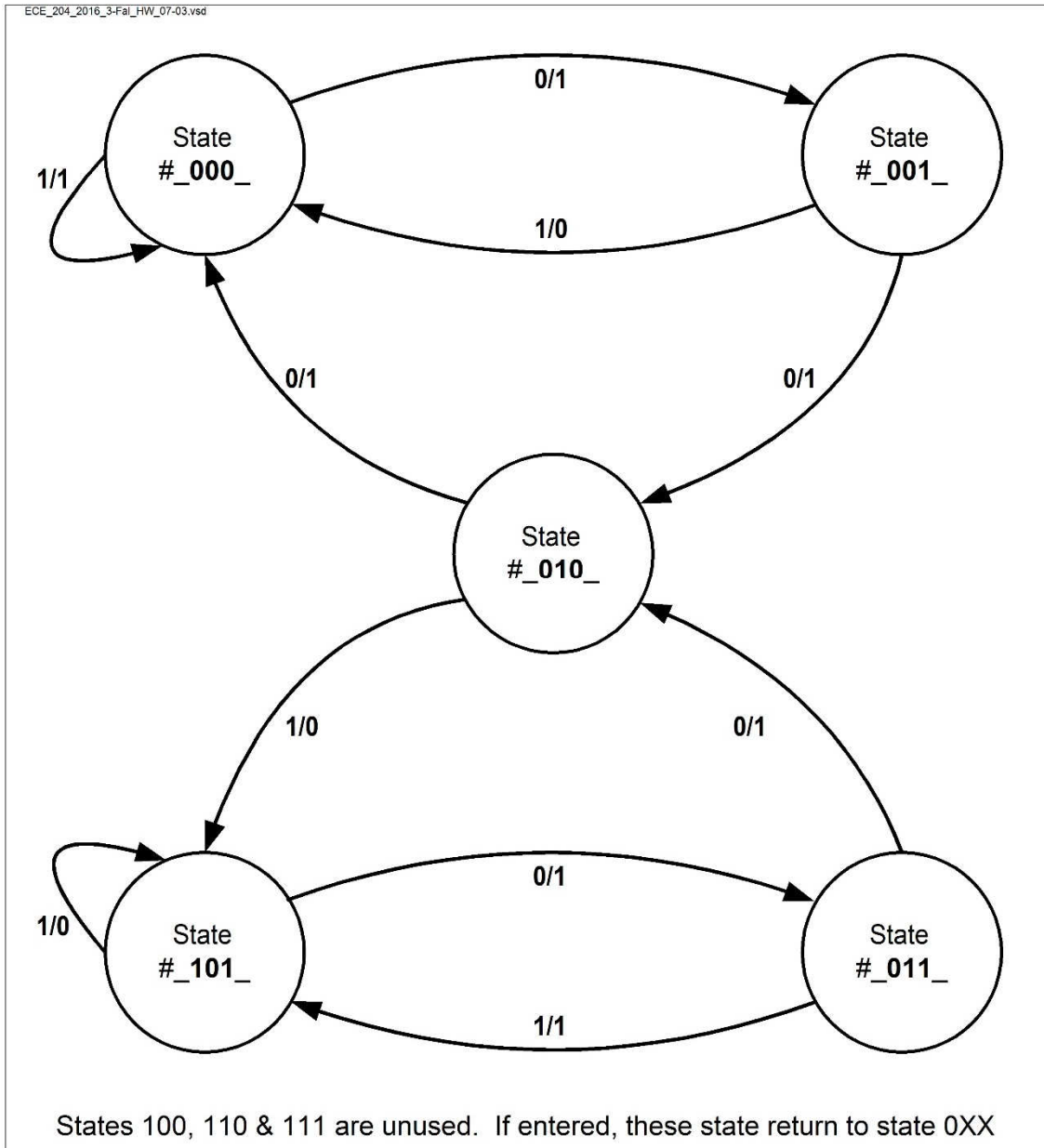5. Given the following state diagram, generate the corresponding state chart including the necessary J and K inputs. Also give the minimized equations for the J and K inputs and for the output. Let the state bits be labeled X, Y and Z , the input A and the output f .



ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

PROBLEM #5, Continued:

X	Y	Z	A	X ⁺	Y ⁺	Z ⁺	<i>f</i>	J _X	K _X	J _Y	K _Y	J _Z	K _Z
0	0	0	0										
0	0	0	1										
0	0	1	0										
0	0	1	1										
0	1	0	0										
0	1	0	1										
0	1	1	0										
0	1	1	1										
1	0	0	0										
1	0	0	1										
1	0	1	0										
1	0	1	1										
1	1	0	0										
1	1	0	1										
1	1	1	0										
1	1	1	1										

XY / ZA	00	01	11	10
00				
01				
11				
10				

XY / ZA	00	01	11	10
00				
01				
11				
10				

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

PROBLEM #5, Continued:

XY / ZA	00	01	11	10
00				
01				
11				
10				

XY / ZA	00	01	11	10
00				
01				
11				
10				

XY / ZA	00	01	11	10
00				
01				
11				
10				

XY / ZA	00	01	11	10
00				
01				
11				
10				

XY / ZA	00	01	11	10
00				
01				
11				
10				

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

6. Design an 8-state state machine counter with the following characteristics:

- If the **e** (even) input is 1, the next state is the next even numbered state (modulo 8).
- If the **e** input is 0, the next state is the next odd numbered state (modulo 8).
- States are encoded using J-K flip-flops labeled **X**, **Y** & **Z** with **X** the MSB.
- The counter has no output other than the state flip-flops.


Give the state table, the state diagram and the minimized equations
For the J and K inputs to each flip-flop.

X	Y	Z	e	X ⁺	Y ⁺	Z ⁺	J _X	K _X	J _Y	K _Y	J _Z	K _Z
0	0	0	0									
0	0	0	1									
0	0	1	0									
0	0	1	1									
0	1	0	0									
0	1	0	1									
0	1	1	0									
0	1	1	1									
1	0	0	0									
1	0	0	1									
1	0	1	0									
1	0	1	1									
1	1	0	0									
1	1	0	1									
1	1	1	0									
1	1	1	1									

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

PROBLEM #6, Continued:

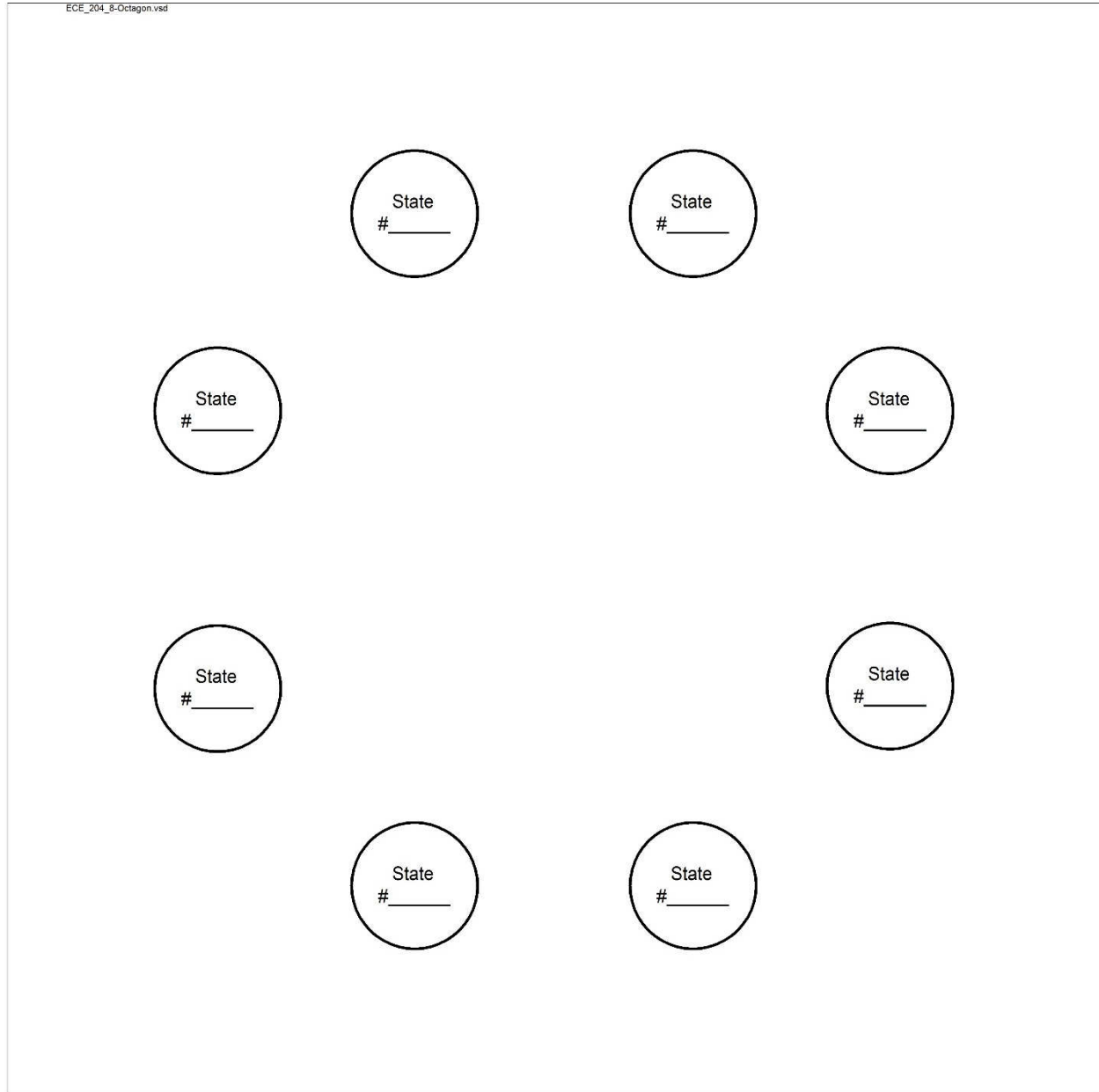

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

PROBLEM #6, Continued:

XY / Ze	00	01	11	10
00				
01				
11				
10				

XY / Ze	00	01	11	10
00				
01				
11				
10				

XY / Ze	00	01	11	10
00				
01				
11				
10				

XY / Ze	00	01	11	10
00				
01				
11				
10				

XY / Ze	00	01	11	10
00				
01				
11				
10				

XY / Ze	00	01	11	10
00				
01				
11				
10				

ECE 204 Introduction to Digital Logic Bill Nelson

Homework #7

7. Draw a five D flip-flop PN counter using an XOR and taps at stages 3 and 5. Do not include forbidden state detection. Show the first 12 successive states assuming the initial state is $\{1,0,0,0,1\}$.