
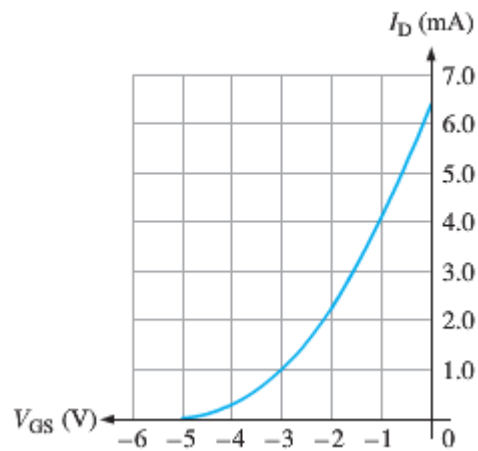


Answer the following questions:

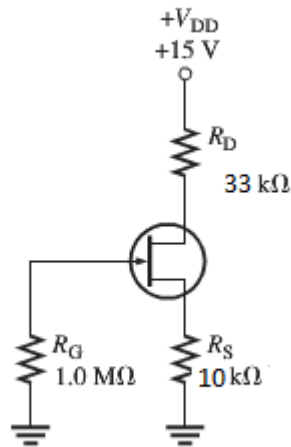
1. What type of transistor has an insulated gate?
2. An  $n$ -channel JFET is biased such that  $V_{GS} = -2$  V using self-bias. The gate resistor is connected to ground.
  - a. What is  $V_S$ ?
  - b. What is the value of  $V_{GS(off)}$  if  $V_P$  is specified to be 6 V?
3. Assume a JFET has the transconductance curve shown in the following figure.
  - a. What is  $I_{DSS}$ ?
  - b. What is  $V_{GS(off)}$ ?
  - c. What is the transconductance at a drain current of 2.0 mA?




4. Assume that the JFET with the transconductance curve shown in the figure for Problem 3 is connected in the circuit shown in the following figure.
  - a. What is  $V_S$ ?
  - b. What is  $I_D$ ?
  - c. What is  $V_{DS}$ ?



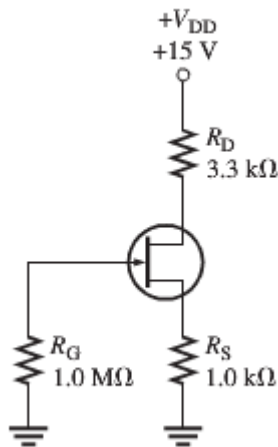
5. Assume that the JFET in the following figure is replaced with one with a lower transconductance.
- What will happen to  $V_{GS}$ ?
  - What will happen to  $V_{DS}$ ?



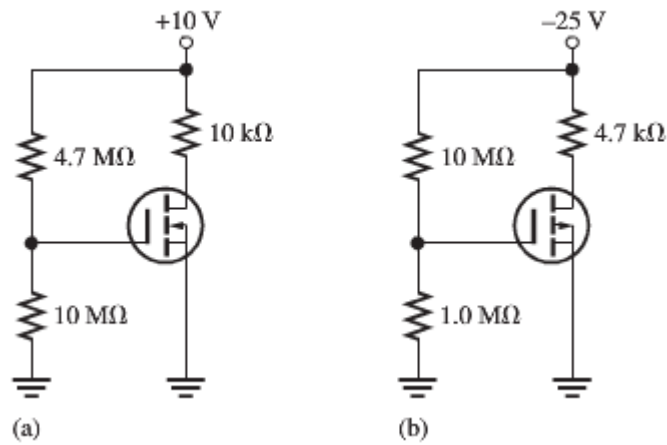- In what mode is an  $n$ -channel D-MOSFET with a positive  $V_{GS}$  operating?
- Each E-MOSFET in the following figure has a  $V_{GS(th)}$  of  $+10 \text{ V}$  or  $-10 \text{ V}$ , depending on whether it is an  $n$ -channel or a  $p$ -channel device. Determine whether each MOSFET is on or off.



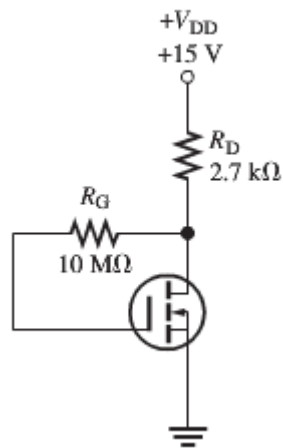8. The drain current for the E-MOSFET shown in the following figure is 3.0 mA. What type of bias is this?
- Can a JFET use this type of bias?
  - Compute the value of  $V_D$ .
  - Compute the value of  $V_G$ .



**Source:** Floyd, T. L., & Buchla, D. M. (2013). *Analog fundamentals: A systems approach* (1st ed.). Upper Saddle River, NJ: Prentice Hall.