

1. Design an op-amp circuit with $R'_1 = 1000\Omega$. $A' = -10$. $R'_o < 10\Omega$.
2. Design an op-amp circuit with $R'_1 > 1M\Omega$. $A' = +10$. $R'_o < 10\Omega$.
3. Two input voltages are $v_1(t)$ and $v_2(t)$. Design an op-amp circuit that will generate the voltage $3v_1(t) - 2v_2(t)$. Its input resistance must exceed $1\text{ k}\Omega$ and its output resistance must be less than 10Ω . Use more than one op-amp if necessary.
- 4.

- 8.9 Consider the inverting amplifier circuit shown in Fig. 8.17. A signal source with Thévenin resistance R_S is to be connected to the input. Calculate the output voltage by two different methods:
- a. By combining R_S and R_1 into a single resistance R'_1 and using Eq. (8.19).
 - b. By finding the input resistance R'_i for the inverting amplifier block and regarding R_S and R'_i as a voltage divider.
- Show that the results obtained via parts (a) and (b) are in agreement.

Figure 8.17:

Another circuit capable of providing voltage amplification is shown in Fig. 8.17. This circuit is known as an *inverting amplifier* because the output has the opposite sign from the input. The voltage amplification is easily found with the ideal-op-amp technique. From Assumption 1 the voltage at the $(-)$ input terminal is taken to be zero. We write a node equation for this point, postulating, from Assumption 2, that no current enters the amplifier terminal.

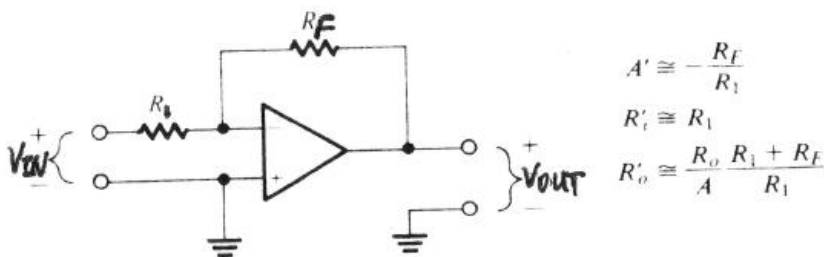


Figure 8.17

Equation 8.19

$$A' = \frac{V_{OUT}}{v_{in}} = -\frac{R_F}{R_1} \text{ (inverting amplifier)}$$

- 5.

- 8.10 Find the open-circuit output voltage of the system shown in Fig. 8.43 as a function of the input voltage v_S .

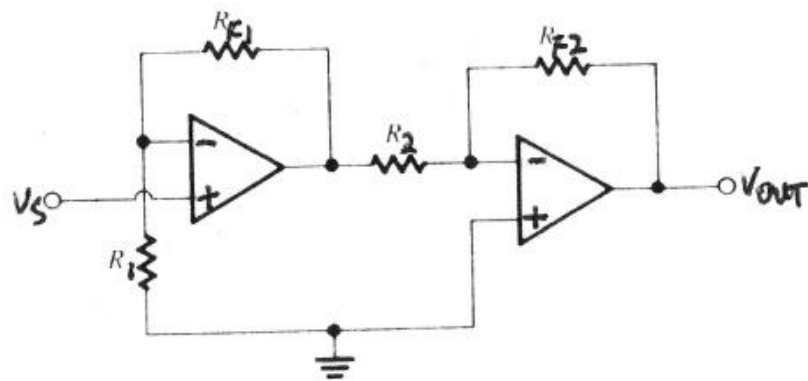


Figure 8.43

6.

- 8.11 In the circuit of Fig. 8.44 find i_L in terms of v_{IN} .

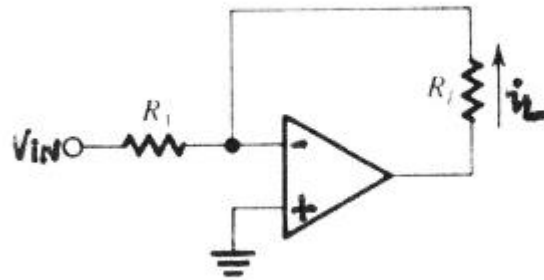


Figure 8.44

7.

- 8.12 In Fig. 8.45, use the ideal-op-amp technique.
 a. Find v_{OUT} as a function of v_{IN} .
 b. What is the voltage at A ?

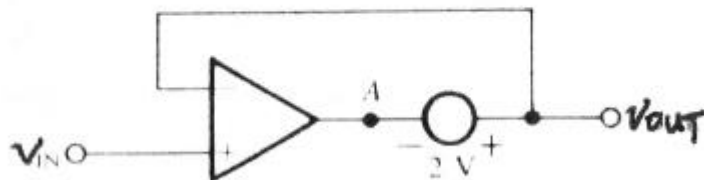


Figure 8.45