
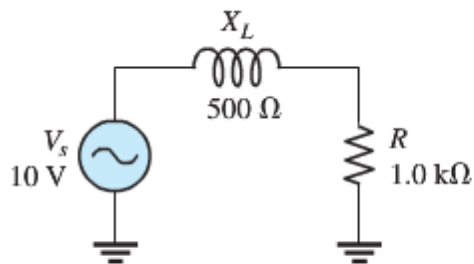


Answer the following questions:

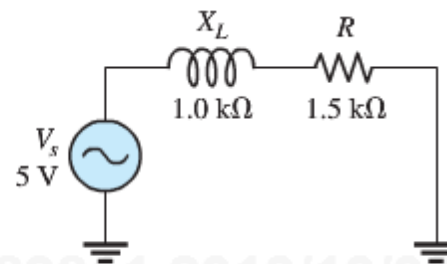1. How much energy is stored by a 100 mH inductor with a current of 1 A?
2. A 15 kHz sinusoidal voltage is applied to a series RL circuit. Determine the frequency of I , V_R , and V_L .
3. Find the impedance of each circuit in the following figures.




(a)



(b)

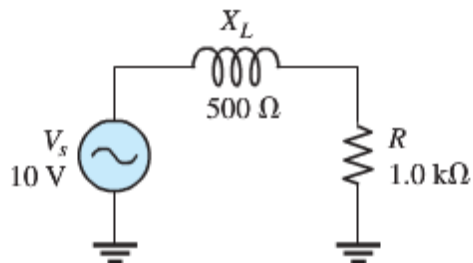
4. Assume that the inductance in the following figure is $796 \mu\text{H}$. What is the source frequency?




(a)

5. Determine the following quantities in the given figure.


- Z
- I_R
- I_L
- I_{tot}
- θ

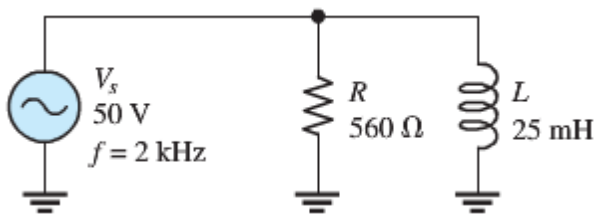

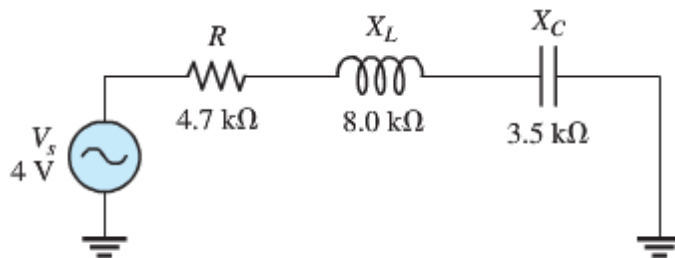
6. Draw the voltage phasor diagram for the circuit in the following figure.



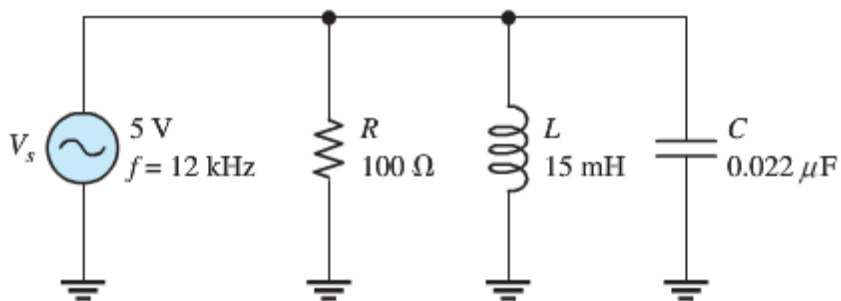7. Is the circuit in the following figure capacitive or inductive? Explain.



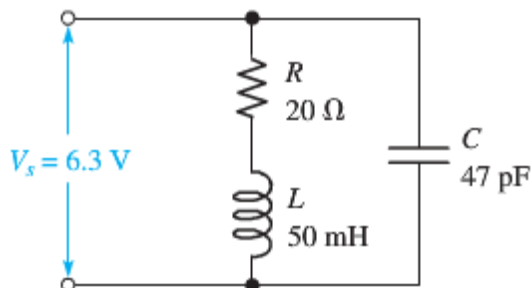8. Find Z at resonance and f_r for the tank circuit in the following figure.



9. At resonance, $X_L = 2 \text{ k}\Omega$ and $R_W = 25 \Omega$ in a parallel resonant band-pass filter. The resonant frequency is 5 kHz. Determine the bandwidth.
10. In a series RL circuit, determine how long it takes the current to build up to its full value for each of the following:
- $R = 56 \Omega$, $L = 50 \mu\text{H}$
 - $R = 3300 \Omega$, $L = 15 \text{ mH}$
 - $R = 22 \text{ k}\Omega$, $L = 100 \text{ mH}$
11. If the lower cutoff frequency is 2400 Hz and the upper cutoff frequency is 2800 Hz, what is the bandwidth?

Source: Floyd, T. L., & Buchla, D. M. (2013). *DC/AC fundamentals: A systems approach* (1st ed.). Upper Saddle River, NJ: Prentice Hall.

Submission Requirements:

Submit your answers in a Microsoft Word document.

The submission should use:

- Font: Arial; 12-point
- Line spacing: Double

Evaluation Criteria:

Your submission will be evaluated against the following criteria:

- Did you include appropriate steps or rationales to determine the answers to questions wherever required?
- Did you correctly answer each question?