


The magnetizing branch of a practical transformer is nonlinear,  $Z_m$  is not constant.

Actual excitation characteristic of TF must be taken into account in determining  $R$ .

Magnetizing characteristic of a typical CT.

(Plot of RMS magnetizing current versus RMS secondary voltage)

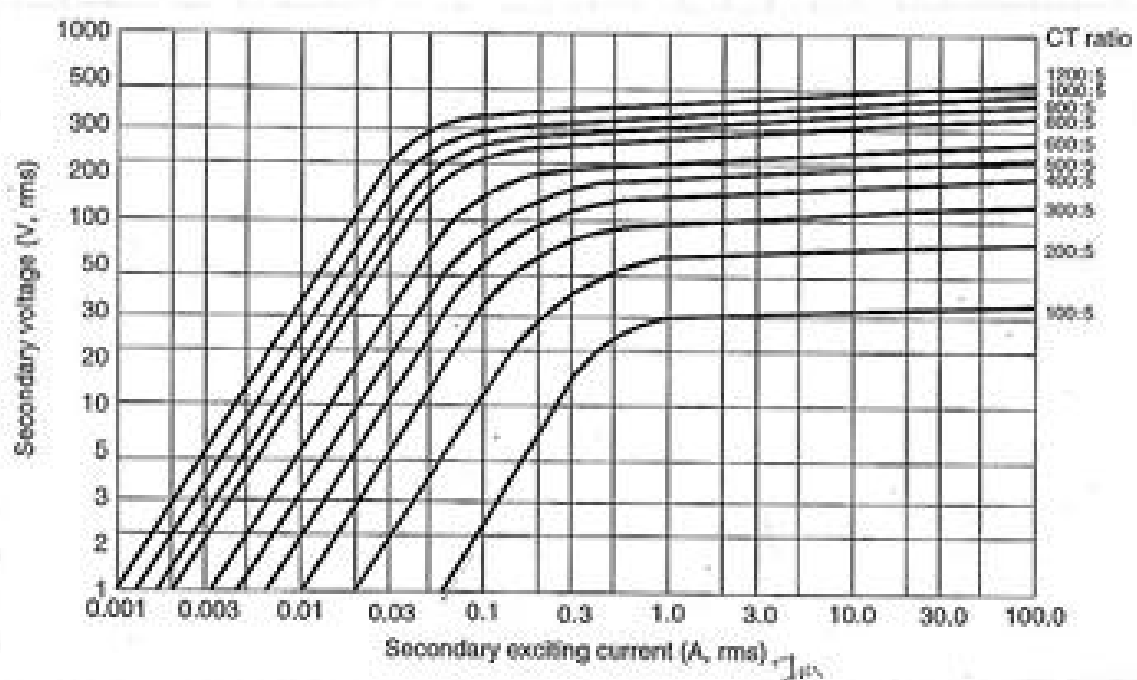$I_m$  for each  $E_m$  must be obtained from this curve, then used in previous equations.



600 : 5 MR	1200 : 5 MR	2000 : 5 MR	3000 : 5 MR
50 : 5	100 : 5	300 : 5	300 : 5
100 : 5	200 : 5	400 : 5	500 : 5
150 : 5	300 : 5	500 : 5	800 : 5
200 : 5	400 : 5	800 : 5	1000 : 5
250 : 5	500 : 5	1100 : 5	1200 : 5
300 : 5	600 : 5	1200 : 5	1500 : 5
400 : 5	800 : 5	1500 : 5	2000 : 5
450 : 5	900 : 5	1600 : 5	2200 : 5
500 : 5	1000 : 5	2000 : 5	2500 : 5
600 : 5	1200 : 5		3000 : 5

MR - Multiratio CT's.

Turns ratios for CT's have been standardized.


Recall: Thévenin equivalent circuits

⇒ consists of a voltage source of

$$41.66 \times (9 + j2) = 384.1 \angle 12.53^\circ$$

in series w/ the burden.

Thévenin equivalent.

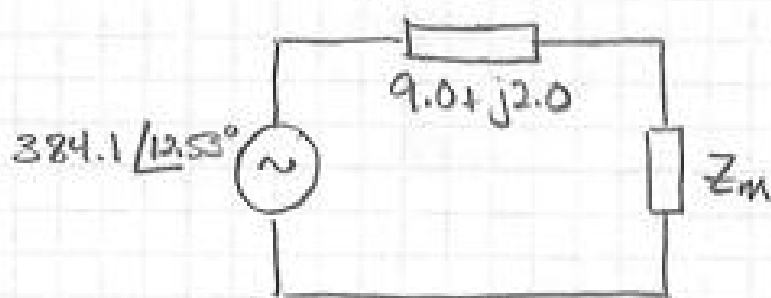

Recall:  $Z_m = |Z_m| \angle 60^\circ$

$$\cos 60 = 0.5$$

$$\sin 60 = 0.866$$

So,

$$Z_m = |Z_m| (0.5 + j0.866)$$

Magnetizing current,  $I_m$ , is

$$I_m = \frac{384.1}{[|Z_m|(0.5 + j0.866) + (9.0 + j2.0)]}$$

$$E_2 = I_m Z_m$$

} \*  
two  
equations w/  
parameter  $Z_m$

For several values of  $|Z_m|$

$ Z_m $	$I_m$	$ E_2 $
$\infty$	0	384.1
100	3.61	361.0
10	21.82	218.2

Superimposing these points on nonlinear curves intersects at

$$I_m = 17A, \bar{E}_2 = 260V$$

Reworking w/ these values yields:

$$\bar{I}_1 = 41.66 \angle 0^\circ$$

$$|Z_m| = \frac{260}{17} = 15.3$$

$$\text{so, } \bar{Z}_m = 15.3 \angle 60^\circ$$

$$I_m = \frac{\bar{I}_1}{9 + j2.0 + \bar{Z}_m} (9 + j2.0)$$

$$= \frac{41.66 \angle 0^\circ}{9 + j2.0 + 15.3 \angle 60^\circ} (9 + j2.0)$$


$$= \frac{384.105 \angle 12.5}{22.58 \angle 42.5} = 17 \angle -29.97^\circ$$

then

$$\bar{I}_2 = \bar{I}_1 - \bar{I}_m$$

$$= 41.66 \angle 0^\circ - 17 \angle -29.97^\circ$$

$$= 28.9 \angle 17.5^\circ$$

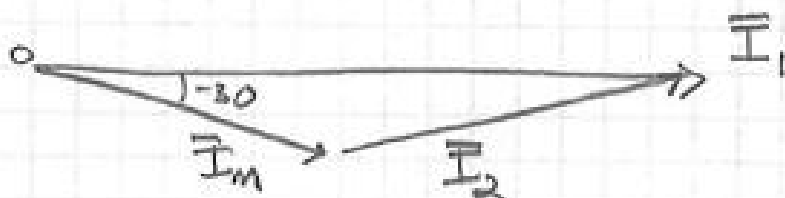

Then,  $e = \frac{H_2 I_m}{H_1}$

$$= \frac{17 \angle -29.97}{41.66 \angle 0^\circ}$$

$$= 0.408 \angle -29.97$$

And

$$R = \frac{1}{1 - e} = \frac{1}{1 - 0.408 \angle -29.97^\circ}$$

$$= 1.47 \angle -17.51^\circ$$

This CT is in severe saturation at this current and at the burden chosen.

In practice, must be used w/ much smaller burdens to provide reasonable accuracies under faulted conditions.