

---

## Transmission Line

- Transfer equation:

$$V_1 = V_2 \cosh(\gamma \ell) + Z_c I_2 \sinh(\gamma \ell)$$

$$I_1 = I_2 \cosh(\gamma \ell) + \frac{V_2}{Z_c} \sinh(\gamma \ell)$$

- Propagation constant:

$$\gamma = \sqrt{yz}$$

- Characteristic impedance:

$$Z_c = \sqrt{\frac{z}{y}} = \frac{z}{\gamma} = \frac{\gamma}{y}$$

- Transmission matrix for  $\Pi$  equivalent circuit:

$$T = \begin{bmatrix} 1 + \frac{ZY}{2} & Z \\ Y(1 + \frac{ZY}{4}) & 1 + \frac{ZY}{2} \end{bmatrix}$$

## Per Unit System

- Impedance base conversion

$$Z_{new,p.u.} = Z_{old,p.u.} \left( \frac{V_{B,old}^l}{V_{B,new}^l} \right)^2 \left( \frac{S_{B,new}^{3\phi}}{S_{B,old}^{3\phi}} \right)$$

Problem 1 [40]

---

1. A 60Hz 50MVA 138kV three-phase transmission line is 300 km-long. The distributed line parameters are

$$r = 0.2\Omega/km, l = 2 mH/km, c = 0.01\mu F/km, g = 0$$

The transmission line delivers its rated power at its rated voltage and at power factor 0.9 lagging.

- Treat the line as “long” transmission line.
  - a. [15] What is the sending-end current?
  
- Treat the line in question 1 as “medium-length” line.
  - b. [10] What is the sending-end voltage and current?
  - c. [5] What is the transmission line efficiency?
  
- Consider it is Surge Impedance Loaded (SIL) (i.e. the line is loaded with its characteristic impedance)
  - d. [6] What are the voltage gain  $|V_2|/|V_1|$  and current gain  $|I_2|/|I_1|$ ?
  - e. [4] What is the driving point impedance  $|V_1|/|I_1|$  of the transmission line?

Problem 2 [35]

---

Consider a power system shown in the figure has the following parameters


Generator:  $30MVA, 13.8kV, X_s = 0.1p.u.$

Load:  $Z_{load} = 40 + j30\Omega$  at each leg of wye connected load

$T_1$ :  $30MVA, 13.2/132kV, X_l = 0.1 p.u.$

$T_2$ :  $20MVA, 138/13.8kV, X_l = 0.08p.u.$

Line:  $j100\Omega$

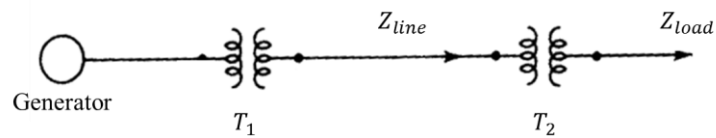

- a. [15] The power base for the system is chosen as  $30MVA$ , and voltage base of the transmission line is  $132kV$ . Using the chosen power and voltage base, define other basis as needed and find the impedance diagram of the power system.
  - If the generator's **terminal voltage** is  $13.2kV$ , find the **actual** values of
    - b. [5] current on transmission line
    - c. [5] voltage at load
    - d. [6] real power delivered to the load and its power factor
    - e. [4] power delivery efficiency of this power system