

Homework #3

1. Problem 1

$$[a] \mathbf{V} = 100\angle -45^\circ \text{ V}, \quad \mathbf{I} = 20\angle 15^\circ \text{ A}$$

Therefore

$$P = \frac{1}{2}(100)(20) \cos[-45 - (15)] = 500 \text{ W}, \quad \text{A} \rightarrow \text{B}$$

$$Q = 1000 \sin -60^\circ = -866.03 \text{ VAR}, \quad \text{B} \rightarrow \text{A}$$

$$[b] \mathbf{V} = 100\angle -45^\circ, \quad \mathbf{I} = 20\angle 165^\circ$$

$$P = 1000 \cos(-210^\circ) = -866.03 \text{ W}, \quad \text{B} \rightarrow \text{A}$$

$$Q = 1000 \sin(-210^\circ) = 500 \text{ VAR}, \quad \text{A} \rightarrow \text{B}$$

$$[c] \mathbf{V} = 100\angle -45^\circ, \quad \mathbf{I} = 20\angle -105^\circ$$

$$P = 1000 \cos(60^\circ) = 500 \text{ W}, \quad \text{A} \rightarrow \text{B}$$

$$Q = 1000 \sin(60^\circ) = 866.03 \text{ VAR}, \quad \text{A} \rightarrow \text{B}$$

$$[d] \mathbf{V} = 100\angle 0^\circ, \quad \mathbf{I} = 20\angle 120^\circ$$

$$P = 1000 \cos(-120^\circ) = -500 \text{ W}, \quad \text{B} \rightarrow \text{A}$$

$$Q = 1000 \sin(-120^\circ) = -866.03 \text{ VAR}, \quad \text{B} \rightarrow \text{A}$$

2. Problem 2

For $v(t) = 3\cos(\omega t + 25^\circ)$ and $i(t) = 5\sin(\omega t - 65^\circ)$, compute the power factor and reactive factor.

$$\text{Ans) PF} = \cos(\theta_v - \theta_i) = \cos(25^\circ - (-155^\circ)) = \cos(180^\circ) = -1$$

$$\text{RF} = \sin(\theta_v - \theta_i) = \sin(25^\circ - (-155^\circ)) = \sin(180^\circ) = 0$$

3. Problem 3

$$\text{From Ex. 9.4 } I_{\text{eff}} = \frac{I_p}{\sqrt{3}} = \frac{0.18}{\sqrt{3}} \text{ A}$$

$$P = I_{\text{eff}}^2 R = \left(\frac{0.0324}{3}\right) (5000) = 54 \text{ W}$$

4. Problem 4 (The problem means that a capacitor of $-j52$ is connected to the load in parallel)

$$[a] Z = (39 + j26)\|(-j52) = 48 - j20 = 52\angle -22.62^\circ \Omega$$

$$\text{Therefore } \mathbf{I}_\ell = \frac{250\angle 0^\circ}{48 - j20 + 1 + j4} = 4.85\angle 18.08^\circ \text{ A(rms)}$$

$$\mathbf{V}_L = Z\mathbf{I}_\ell = (52\angle -22.62^\circ)(4.85\angle 18.08^\circ) = 252.20\angle -4.54^\circ \text{ V(rms)}$$


$$\mathbf{I}_L = \frac{\mathbf{V}_L}{39 + j26} = 5.38\angle -38.23^\circ \text{ A(rms)}$$

- [b] $S_L = \mathbf{V}_L \mathbf{I}_L^* = (252.20 \angle -4.54^\circ)(5.38 \angle +38.23^\circ) = 1357 \angle 33.69^\circ$
 $= (1129.09 + j752.73) \text{ VA}$
 $P_L = 1129.09 \text{ W}; \quad Q_L = 752.73 \text{ VAR}$
- [c] $P_\ell = |\mathbf{I}_\ell|^2 1 = (4.85)^2 \cdot 1 = 23.52 \text{ W}; \quad Q_\ell = |\mathbf{I}_\ell|^2 4 = 94.09 \text{ VAR}$
- [d] $S_g(\text{delivering}) = 250 \mathbf{I}_g^* = (1152.62 - j376.36) \text{ VA}$
 Therefore the source is delivering 1152.62 W and absorbing 376.36 magnetizing VAR.
- [e] $Q_{\text{cap}} = \frac{|\mathbf{V}_L|^2}{-52} = \frac{(252.20)^2}{-52} = -1223.18 \text{ VAR}$
 Therefore the capacitor is delivering 1223.18 magnetizing VAR.
- Check: $94.09 + 752.73 + 376.36 = 1223.18 \text{ VAR}$ and
 $1129.09 + 23.52 = 1152.62 \text{ W}$


5. Problem 5

- [a] The phasor domain equivalent circuit and the Thévenin equivalent are shown below:

Phasor domain equivalent circuit:

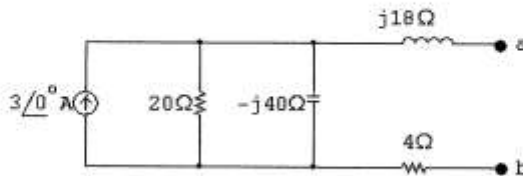

Thévenin equivalent:

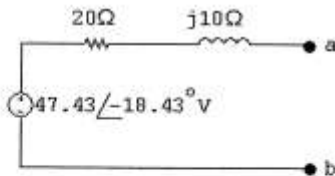

$$\mathbf{V}_{\text{Th}} = 3 \frac{-j800}{20 - j40} = 48 - j24 = 53.67 \angle -26.57^\circ \text{ V}$$

$$\mathbf{Z}_{\text{Th}} = 4 + j18 + \frac{-j800}{20 - j40} = 20 + j10 = 22.36 \angle 26.57^\circ \Omega$$

For maximum power transfer, $\mathbf{Z}_L = (20 - j10) \Omega$

$$[\text{b}] \mathbf{I} = \frac{53.67 \angle -26.57^\circ}{40} = 1.34 \angle -26.57^\circ \text{ A}$$

$$\text{Therefore } P = \left(\frac{1.34}{\sqrt{2}} \right)^2 20 = 17.96 \text{ W}$$


$$[\text{c}] R_L = |\mathbf{Z}_{\text{Th}}| = 22.36 \Omega$$

$$[\text{d}] \mathbf{I} = \frac{53.67 \angle -26.57^\circ}{42.36 + j10} = 1.23 \angle -39.85^\circ \text{ A}$$

$$\text{Therefore } P = \left(\frac{1.23}{\sqrt{2}} \right)^2 (22.36) = 17 \text{ W}$$

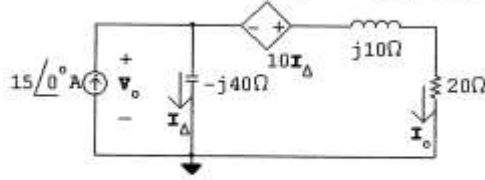6. Problem 6

$$j\omega L = j10,000(10^{-3}) = j10\Omega; \quad \frac{1}{j\omega C} = \frac{10^6}{j10,000(2.5)} = -j40\Omega$$



$$-15 + \frac{V_o}{-j40} + \frac{V_o + 10(V_o / -j40)}{20 + j10} = 0$$

$$\therefore V_o \left[\frac{1}{-j40} + \frac{1 + j0.25}{20 + j10} \right] = 15$$

$$\therefore V_o = 300 - j100 \text{ V}$$

$$\therefore I_{\Delta} = \frac{V_o}{-j40} = 2.5 + j7.5 \text{ A}$$


$$I_o = 15\angle 0^\circ - I_{\Delta} = 15 - 2.5 - j7.5 = 12.5 - j7.5 = 14.58\angle -30.9^\circ \text{ A}$$

$$P_{20\Omega} = \frac{1}{2} |I_o|^2 20 = 2125 \text{ W}$$

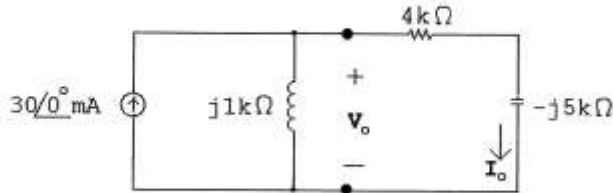7. Problem 7

$$I_o = 30\angle 0^\circ \text{ mA}$$

$$j\omega L = j(100)(10) = j1000\Omega; \quad \frac{1}{j\omega C} = \frac{10^6}{j(100)(2)} = -j5000\Omega$$



$$I_o = \frac{30\angle 0^\circ (j1000)}{4000 - j4000} = 3.75\sqrt{2}\angle 135^\circ \text{ mA}$$

$$P = |I_o|_{\text{rms}}^2 (4000) = (3.75)^2 (4000) = 56.25 \text{ mW}$$

$$Q = |I_o|_{\text{rms}}^2 (-5000) = -70.3125 \text{ mVAR}$$

$$S = P + jQ = 56.25 - j70.3125 \text{ mVA}$$

$$|S| = 90.044 \text{ mVA}$$