



**Office of Continuing & Distance Education  
College of Engineering  
The Pennsylvania State University  
301-A Engineering Unit C  
University Park, PA 16802  
(814) 865-7643**

You are receiving this exam for a student enrolled in EE 211/212 at Penn State University.

**PLEASE NOTE:**

The student has a maximum of **1 1/2 Hours (90 Minutes)** to complete the exam. The examination is **closed book/notes. Calculators are permitted.**

**The use of any Cell Phone or electronic device during this exam is prohibited.**

**Proctor: Please complete the information below and return this form with the Exam.**

\_\_\_\_\_  
Student Name (Please Print)

\_\_\_\_\_  
Proctor Name (Please Print)

\_\_\_\_\_  
Student Signature

\_\_\_\_\_  
Proctor Signature

Date: \_\_\_\_\_

Start Time: \_\_\_\_\_

End Time: \_\_\_\_\_

If you have an administration question, please contact Alex Zimmerman at the above number or by email at [alz@engr.psu.edu](mailto:alz@engr.psu.edu)

Thank you for agreeing to be a proctor.

*Alex Zimmerman*


Alex Zimmerman  
College of Engineering

Circle or check off the correct answers in this exam.

Name: \_\_\_\_\_

**Problem 1**

1.

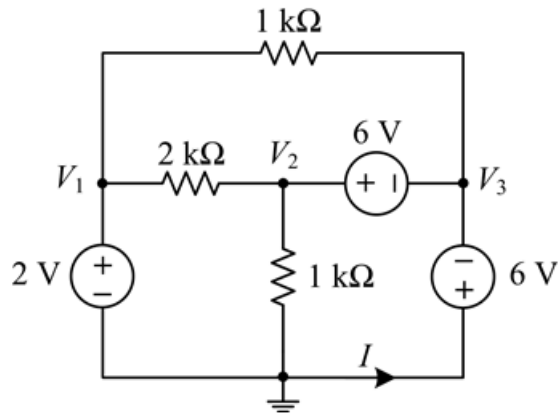


Using nodal analysis, solve for the current  $I$ .

- A) -9 mA
- B) 9 mA
- C) -12 mA
- D) 0 mA
- E) 12 mA

## Problem 2

2.

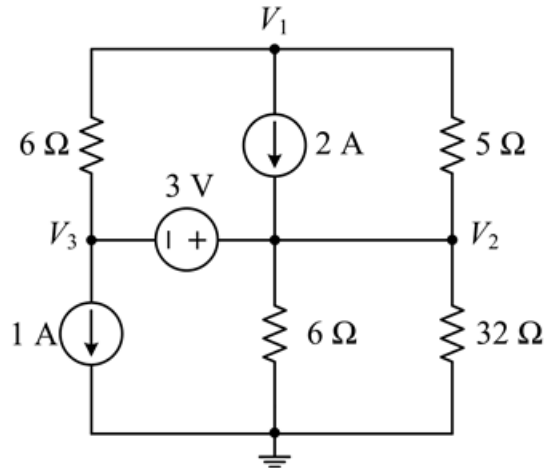


The supernode used to solve this circuit is located between which two nodes?

- A)  $V_3$  and Ground
- B)  $V_1$  and  $V_3$
- C)  $V_2$  and  $V_3$
- D)  $V_1$  and  $V_2$
- E)  $V_2$  and Ground

Problem 3

3.

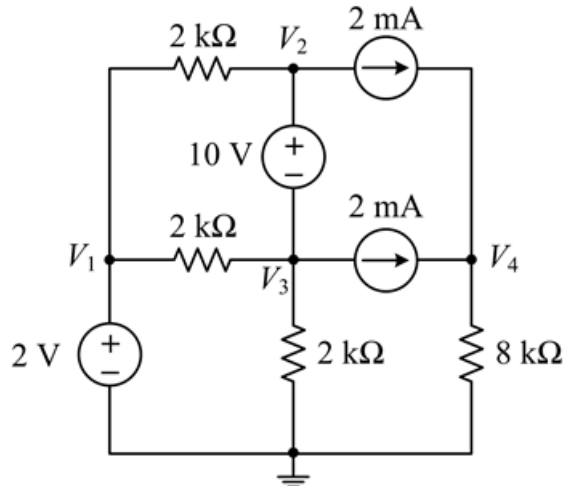


Solve for the voltages  $V_2$  and  $V_3$  in the above circuit.

- A)  $V_2 = 4.33 \text{ V}$  and  $V_3 = -5.67 \text{ V}$
- B)  $V_2 = 7.33 \text{ V}$  and  $V_3 = -2.67 \text{ V}$
- C)  $V_2 = 5.33 \text{ V}$  and  $V_3 = -4.67 \text{ V}$
- D)  $V_2 = 15.67 \text{ V}$  and  $V_3 = 5.57 \text{ V}$
- E)  $V_2 = 14.67 \text{ V}$  and  $V_3 = 4.67 \text{ V}$

## Problem 4

4.

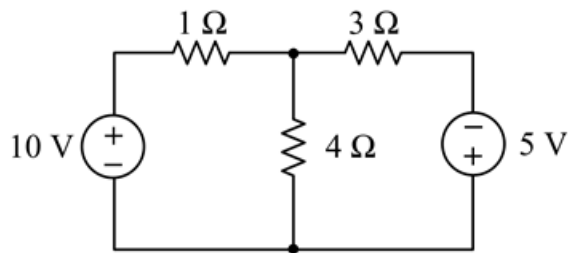


Solve for the voltage drop across the 4 ohm resistor.

- A) 3.75 V
- B) 7.5 V
- C) 5.94 V
- D) 5.26 V
- E) 0 V

## Problem 5

5.

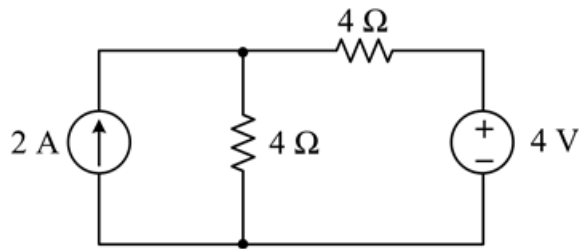


Find the power supplied by the 2A source.

- A) -12 W
- B) -2 W
- C) 18 W
- D) 12 W
- E) 2 W

## Problem 6

6.

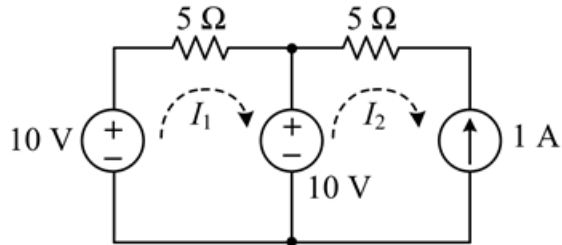


Solve for the currents  $I_1$  and  $I_2$  in the above circuit.

- A)  $I_1 = -2$  A and  $I_2 = 1$  A
- B)  $I_1 = 0.5$  A and  $I_2 = -1$  A
- C)  $I_1 = -2$  A and  $I_2 = -1$  A
- D)  $I_1 = 0$  A and  $I_2 = 1$  A
- E)  $I_1 = 0$  A and  $I_2 = -1$  A

Problem 7

7.

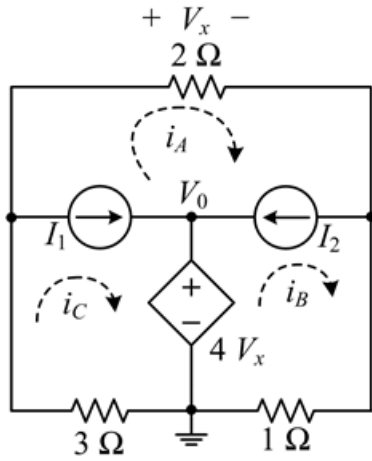


Which of the following answers describes the supermesh equation for the circuit shown above?

- A)  $2i_A - i_B - 3i_C = 0$
- B)  $2i_A + i_B + i_C = 0$
- C)  $-2i_A + i_B - 3i_C = 0$
- D)  $i_A + i_B + 3i_C = 0$
- E)  $2i_A + i_B + 3i_C = 0$



## Problem 8

8.

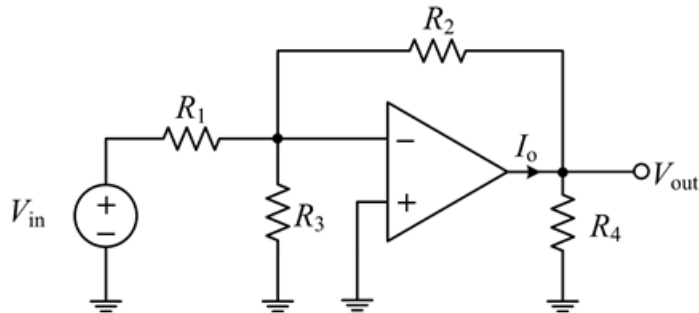


Which resistor(s) affect(s) the gain  $V_{out}/V_{in}$ ?

- A)  $R_4$
- B)  $R_3$
- C)  $R_1$  and  $R_2$
- D)  $R_1$ ,  $R_2$ , and  $R_3$
- E)  $R_1$

## Problem 9

9.

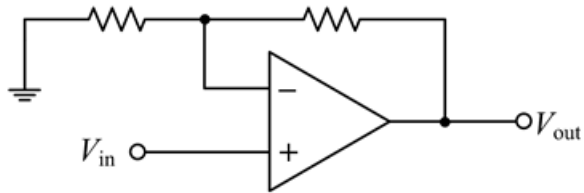


Which answer best describes the function of the above circuit?

- A) Inverting amplifier
- B) Unity-gain buffer
- C) Difference amplifier
- D) Inverting summer
- E) Noninverting amplifier

## Problem 10

10.

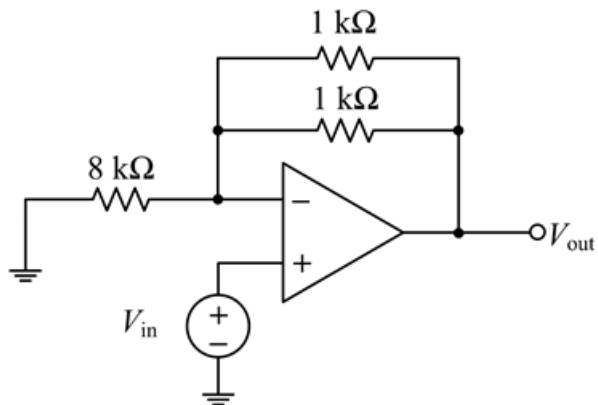


Solve for the gain,  $V_{out}/V_{in}$ , of the circuit above.

Assume that the op amp is ideal and is operating in its linear region.

- A) 0.125 V/V
- B) 1.0625 V/V
- C) 1.125 V/V
- D) 1 V/V
- E) 0.0625 V/V

## Problem 11

11.

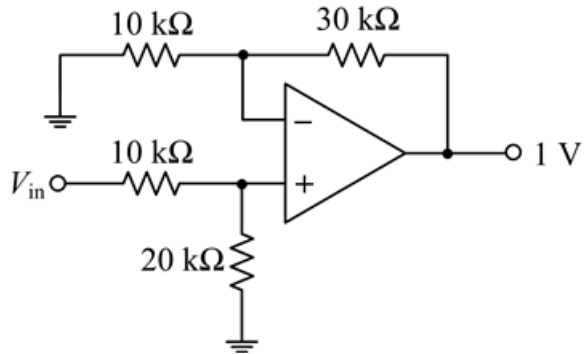


Which of the following input voltage values produce 1V at the op-amp output?  
Assume that the op-amp is ideal and is operating in its linear region.

- A) 0.75 V
- B) 0.6 V
- C) 1 V
- D) 0 V
- E) 0.375 V

## Problem 12

12.

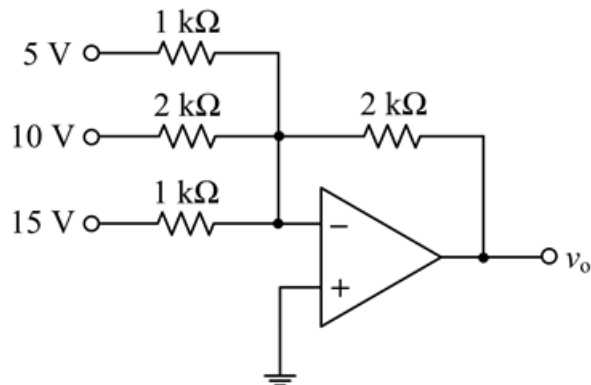


Solve for the value of  $v_o$  in the circuit above.

Assume that the op-amp is ideal and is operating in its linear region.

- A)  $-25\text{ V}$
- B)  $25\text{ V}$
- C)  $-50\text{ V}$
- D)  $75\text{ V}$
- E)  $50\text{ V}$

## Problem 13

13.

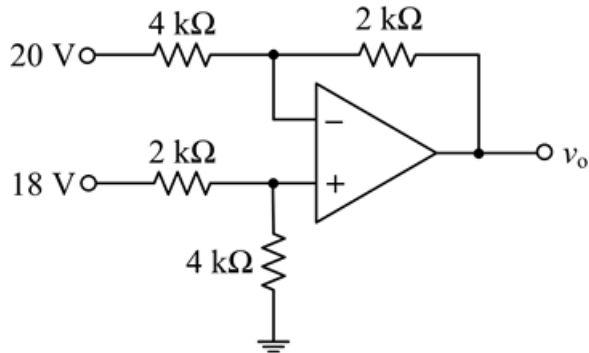


Solve for the value of  $v_o$  in the circuit above.

Assume that the op-amp is ideal and is operating in its linear region.

- A) 4 V
- B) 2 V
- C) 1 V
- D) 8 V
- E) 6 V

## Problem 14

14.

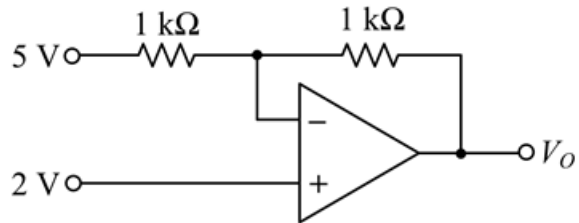


Determine the value of  $v_o$ , given the input voltages shown.

Assume that the op amp is ideal and is operating in the linear region.

- A) -1 V
- B) 10 V
- C) -2 V
- D) 0 V
- E) -5 V

Problem 15

15.

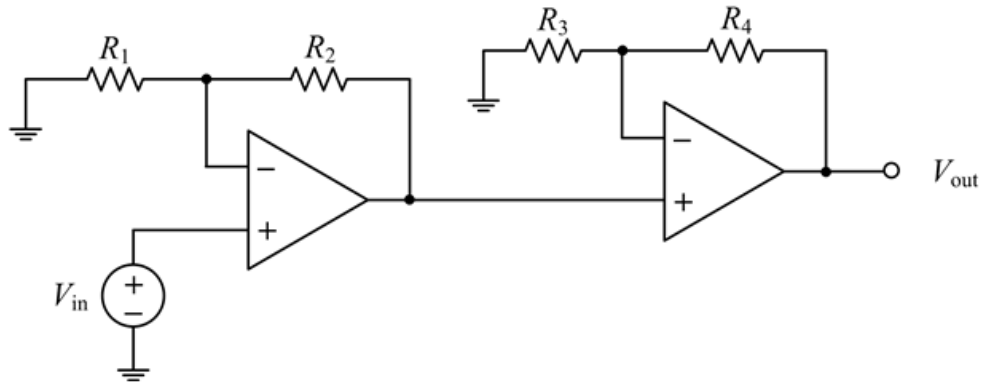


Which resistor values result in a circuit gain,  $V_{out}/V_{in}$ , of +5000 V/V?

- A)  $R_1 = 500 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$ ,  $R_4 = 1 \text{ k}\Omega$
- B)  $R_1 = 499 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ ,  $R_3 = 9 \text{ k}\Omega$ ,  $R_4 = 1 \text{ k}\Omega$
- C)  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 500 \text{ k}\Omega$ ,  $R_3 = 1 \text{ k}\Omega$ ,  $R_4 = 10 \text{ k}\Omega$
- D) None of the following are correct
- E)  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 499 \text{ k}\Omega$ ,  $R_3 = 1 \text{ k}\Omega$ ,  $R_4 = 9 \text{ k}\Omega$



## Problem 16

16.

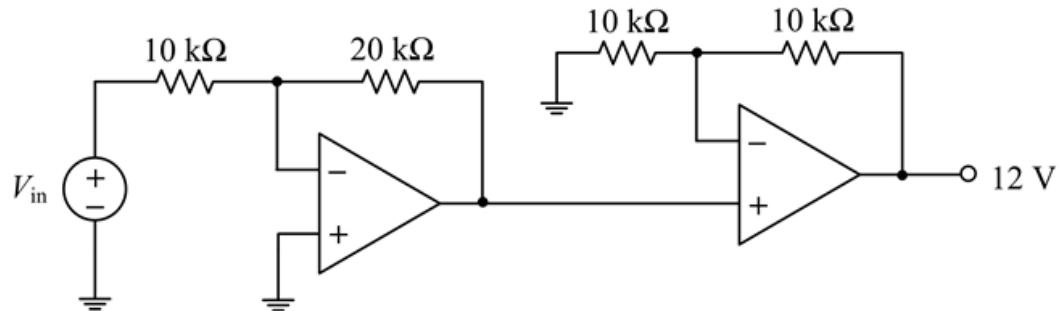


Solve for the value of  $V_{in}$  needed to produce  $12\text{ V}$  at the output.

Assume that the op-amps are ideal and are operating in their linear regions.

- A)  $6\text{ V}$
- B)  $-6\text{ V}$
- C)  $0\text{ V}$
- D)  $3\text{ V}$
- E)  $-3\text{ V}$

## Problem 17

17.

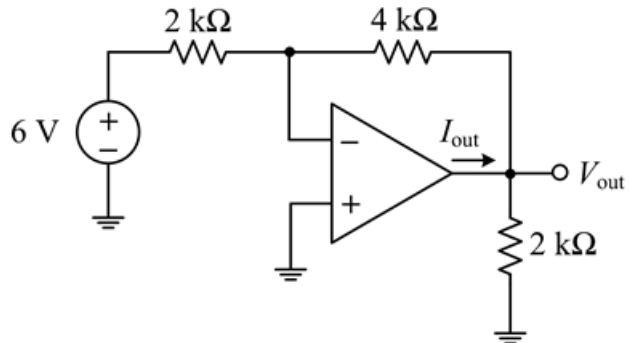


Determine the power supplied by the op-amp in the circuit above.  
Assume that the op-amp is ideal and is operating in its linear region.

- A) -120 mW
- B) 108 mW
- C) 0 W
- D) 120 mW
- E) -108 mW

## Problem 18

18.

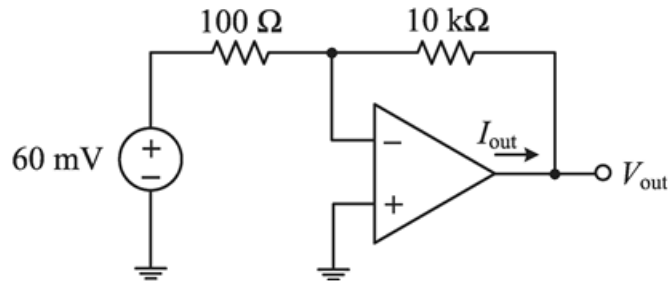


Determine the power supplied by the op-amp in the circuit above.  
Assume that the op-amp is ideal and is operating in its linear region.

- A) 6.4 mW
- B) 1.6 mW
- C) 0 W
- D) 3.6 mW
- E) 8 mW

## Problem 19

19.

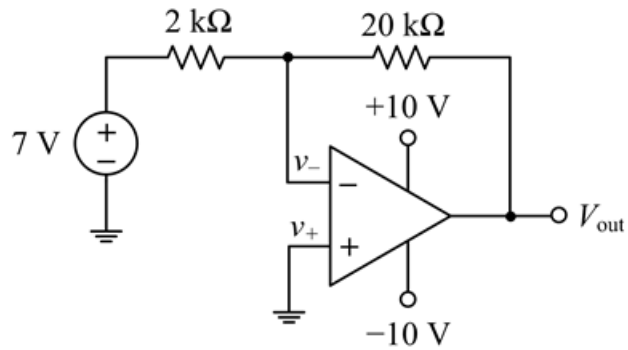


The op amp in the above circuit is ideal and has a saturation voltage of  $\pm 10\text{ V}$ . Solve for the voltage,  $v_-$ , at the inverting input terminal.

- A)  $-5.45\text{ V}$
- B)  $-10\text{ V}$
- C)  $5.45\text{ V}$
- D)  $10\text{ V}$
- E)  $0\text{ V}$
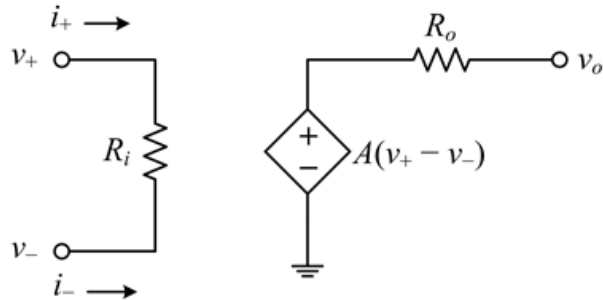
## Problem 20-24

This last question consists of five true/false sub-parts, 1 point each. All questions refer to the op amp model shown in the figure below:



20. In an ideal op amp the input currents  $i_+$  and  $i_-$  are zero amperes.
- A) True  
 B) False
21. In an ideal op amp the gain,  $A$ , is infinite.
- A) True  
 B) False
22. In an ideal op amp the output resistance,  $R_o$ , is infinite.
- A) True  
 B) False
23. In an ideal op amp when negative feedback is applied and when the op amp is not in saturation, the input voltages  $v_+$  and  $v_-$  are equal.
- A) True  
 B) False
24. In an ideal op amp the input resistance,  $R_i$ , is zero ohms.
- A) True  
 B) False